

Advanced Analog Building Blocks

Stability & Compensation



Wei SHEN (KIP)

Bode Plot



UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386

- real zeros
- zeros with complex conjugates
- real poles
- poles with complex conjugates


<http://lipsa.swarthmore.edu/Bode/Bode.html>

Term	Magnitude	Phase
Constant: K	$20\log_{10}(K)$	K>0: 0° K<0: $\pm 180^\circ$
Pole at Origin (Integrator) $\frac{1}{s}$	-20 dB/decade passing through 0 dB at $\omega=1$	-90°
Zero at Origin (Differentiator) s	+20 dB/decade passing through 0 dB at $\omega=1$ <i>(Mirror image of Integrator about 0 dB)</i>	+90° <i>(Mirror image of Integrator about 0°)</i>
Real Pole $\frac{1}{\frac{s}{\omega_0} + 1}$	1. Draw low frequency asymptote at 0 dB 2. Draw high frequency asymptote at -20 dB/decade 3. Connect lines at ω_0 .	1. Draw low frequency asymptote at 0° 2. Draw high frequency asymptote at -90° 3. Connect with a straight line from $0.1 \cdot \omega_0$ to $10 \cdot \omega_0$
Real Zero $\frac{s}{\omega_0} + 1$	1. Draw low frequency asymptote at 0 dB 2. Draw high frequency asymptote at +20 dB/decade 3. Connect lines at ω_0 . <i>(Mirror image of Real Pole about 0 dB)</i>	1. Draw low frequency asymptote at 0° 2. Draw high frequency asymptote at $+90^\circ$ 3. Connect with a straight line from $0.1 \cdot \omega_0$ to $10 \cdot \omega_0$ <i>(Mirror image of Real Pole about 0°)</i>
Underdamped Poles (Complex conjugate poles) $\frac{1}{\left(\frac{s}{\omega_0}\right)^2 + 2\zeta\left(\frac{s}{\omega_0}\right) + 1}$ $0 < \zeta < 1$	1. Draw low frequency asymptote at 0 dB 2. Draw high frequency asymptote at -40 dB/decade 3. If $\zeta < 0.5$, then draw peak at ω_0 with amplitude $ H(j\omega_0) = -20 \cdot \log_{10}(2\zeta)$, else don't draw peak 4. Connect lines	1. Draw low frequency asymptote at 0° 2. Draw high frequency asymptote at -180° 3. Connect with straight line from $\omega = \frac{\omega_0}{10^\zeta}$ to $\omega_0 \cdot 10^\zeta$ <i>You can also look in a textbook for examples</i>
Underdamped Zeros (Complex conjugate zeros) $\left(\frac{s}{\omega_0}\right)^2 + 2\zeta\left(\frac{s}{\omega_0}\right) + 1$ $0 < \zeta < 1$	1. Draw low frequency asymptote at 0 dB 2. Draw high frequency asymptote at +40 dB/decade 3. If $\zeta < 0.5$, then draw peak at ω_0 with amplitude $ H(j\omega_0) = +20 \cdot \log_{10}(2\zeta)$, else don't draw peak 4. Connect lines <i>(Mirror image of Underdamped Pole about 0 dB)</i>	1. Draw low frequency asymptote at 0° 2. Draw high frequency asymptote at $+180^\circ$ 3. Connect with straight line from $\omega = \frac{\omega_0}{10^\zeta}$ to $\omega_0 \cdot 10^\zeta$ <i>You can also look in a textbook for examples.</i> <i>(Mirror image of Underdamped Pole about 0°)</i>

Bode Plot – example




Magnitude Plot

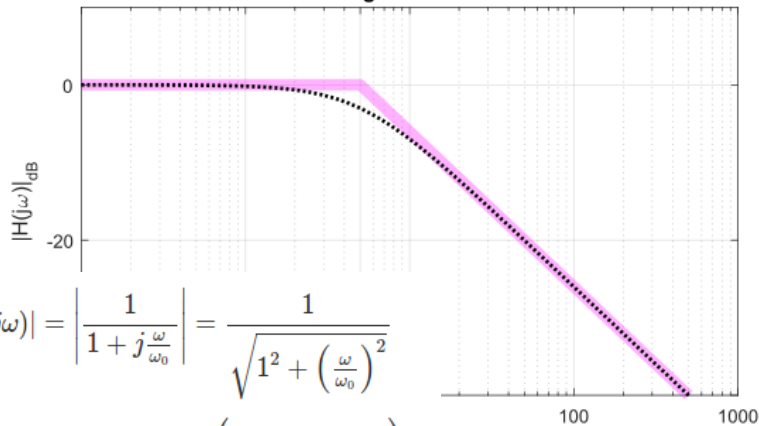

$$|H(j\omega)| = \left| \frac{1}{1 + j\frac{\omega}{\omega_0}} \right| = \frac{1}{\sqrt{1^2 + \left(\frac{\omega}{\omega_0}\right)^2}}$$

$$|H(j\omega)|_{dB} = 20 \cdot \log_{10} \left(\frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}} \right)$$

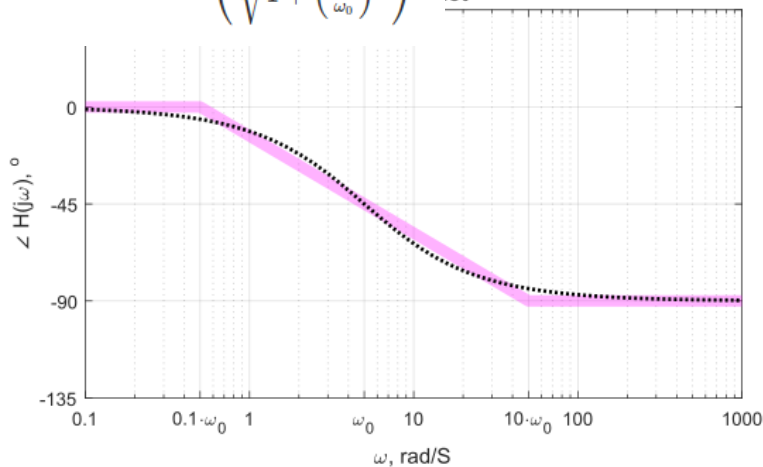

Real Poles :

$$\frac{1}{\frac{s}{\omega_0} + 1}$$

Amplitude

- Draw low frequency asymptote at 0 dB
- Draw high frequency asymptote at -20 dB/decade
- Connect lines at ω_0 .

Phase

- Draw low frequency asymptote at 0°
- Draw high frequency asymptote at -90°
- Connect with a straight line from $0.1 \cdot \omega_0$ to $10 \cdot \omega_0$

Second Order Real Poles :

$$\frac{1}{\left(\frac{s}{\omega_0} + 1\right)^2}$$

Amplitude

- Draw low frequency asymptote at 0 dB
- Draw high frequency asymptote at -40 dB/decade
- Connect lines at break frequency.

Phase

- Draw low frequency asymptote at 0°
- Draw high frequency asymptote at -180°
- Connect with a straight line from $0.1 \cdot \omega_0$ to $10 \cdot \omega_0$

Bode Plot – example



Real Negative Zeros :




$$\frac{s}{\omega_0} + 1$$

Amplitude

- Draw low frequency asymptote at 0 dB
- Draw high frequency asymptote at +20 dB/decade
- Connect lines at ω_0 .

Phase

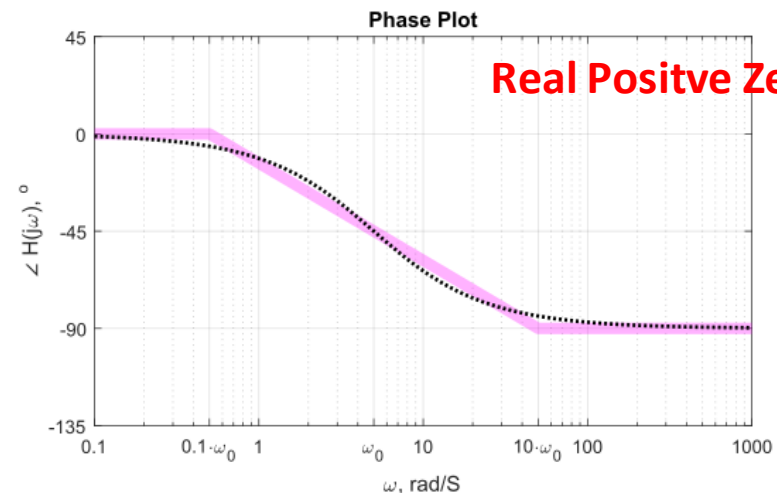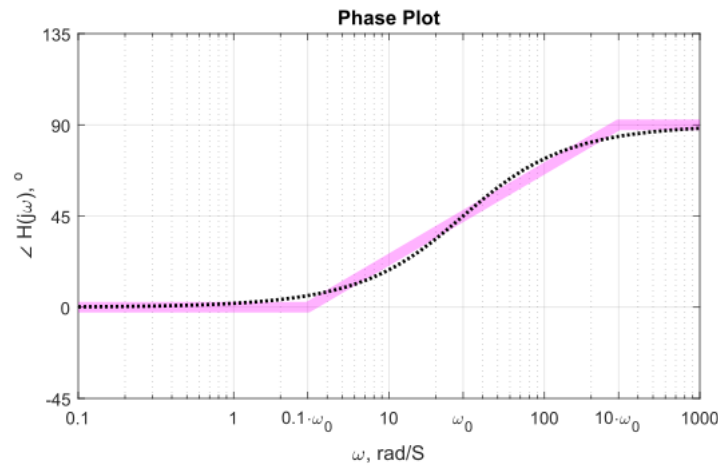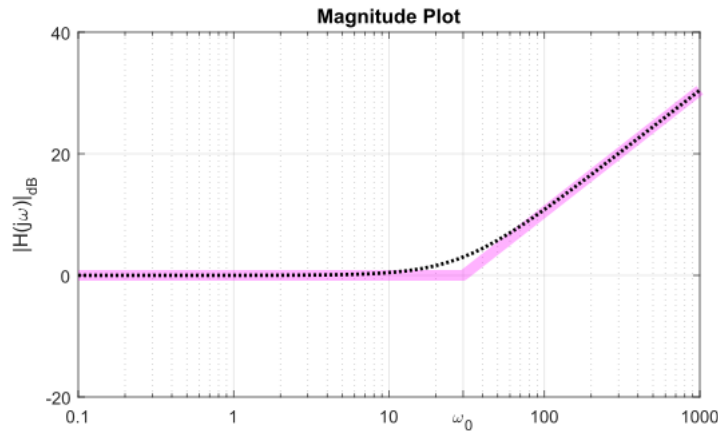- Draw low frequency asymptote at 0°
- Draw high frequency asymptote at $+90^\circ$
- Connect with a straight line from $0.1 \cdot \omega_0$ to $10 \cdot \omega_0$



Real Positive Zeros :

Bode Plot – example



$$H(s) = \frac{\omega_0^2}{s^2 + 2\zeta\omega_0 s + \omega_0^2} = \frac{1}{\left(\frac{s}{\omega_0}\right)^2 + 2\zeta\left(\frac{s}{\omega_0}\right) + 1}$$

Complex Conjugate Poles :

Amplitude:

$$\begin{aligned} |H(j\omega)| &= \left| \frac{1}{\left(\frac{j\omega}{\omega_0}\right)^2 + 2\zeta\left(\frac{j\omega}{\omega_0}\right) + 1} \right| = \left| \frac{1}{-\left(\frac{\omega}{\omega_0}\right)^2 + j2\zeta\left(\frac{\omega}{\omega_0}\right) + 1} \right| = \left| \frac{1}{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right) + j\left(2\zeta\left(\frac{\omega}{\omega_0}\right)\right)} \right| \\ &= \frac{1}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \left(2\zeta\frac{\omega}{\omega_0}\right)^2}} \end{aligned}$$

$$|H(j\omega)|_{dB} = -20 \cdot \log_{10} \left(\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \left(2\zeta\frac{\omega}{\omega_0}\right)^2} \right)$$

Phase:

$$\begin{aligned} \angle H(j\omega) &= \angle \left(\frac{1}{\left(\frac{j\omega}{\omega_0}\right)^2 + 2\zeta\left(\frac{j\omega}{\omega_0}\right) + 1} \right) = -\angle \left(\left(\frac{j\omega}{\omega_0}\right)^2 + 2\zeta\left(\frac{j\omega}{\omega_0}\right) + 1 \right) = -\angle \left(1 - \left(\frac{\omega}{\omega_0}\right)^2 + j2\zeta\left(\frac{\omega}{\omega_0}\right) \right) \\ &= -\arctan \left(\frac{2\zeta\frac{\omega}{\omega_0}}{1 - \left(\frac{\omega}{\omega_0}\right)^2} \right) \end{aligned}$$

Bode Plot – example



Complex Conjugate Poles :


Amplitude

- Draw low frequency asymptote at 0 dB
- Draw high frequency asymptote at -40 dB/decade
- If $\zeta < 0.5$, then draw peak at ω_0 with amplitude $|H(j\omega_0)| = -20 \cdot \log_{10}(2\zeta)$, else don't draw peak
- Connect lines


Phase

- Draw low frequency asymptote at 0°
- Draw high frequency asymptote at -180°
- Connect with straight line from $\omega_0 / 10^\zeta$ to $\omega_0 * 10^\zeta$


Magnitude

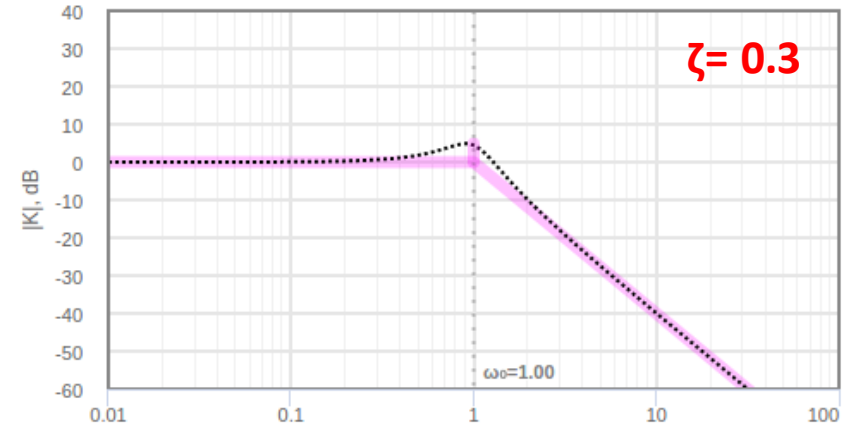


Phase

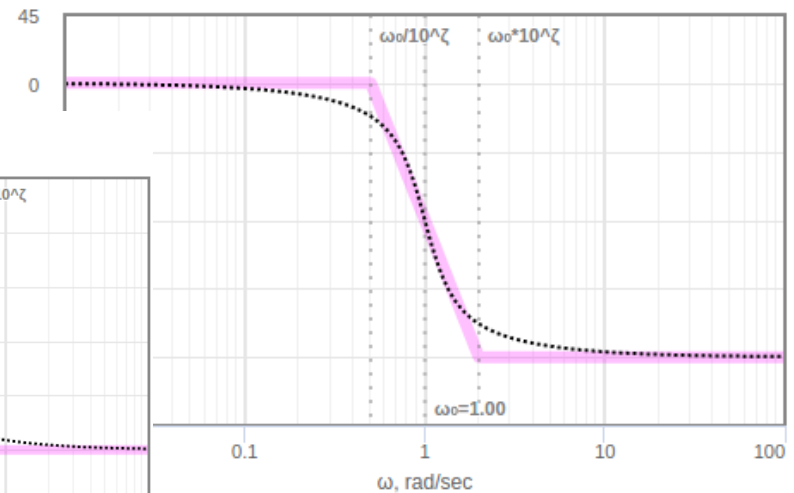

Magnitude

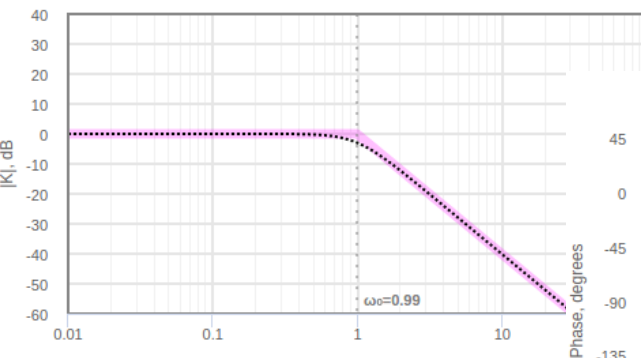


Phase

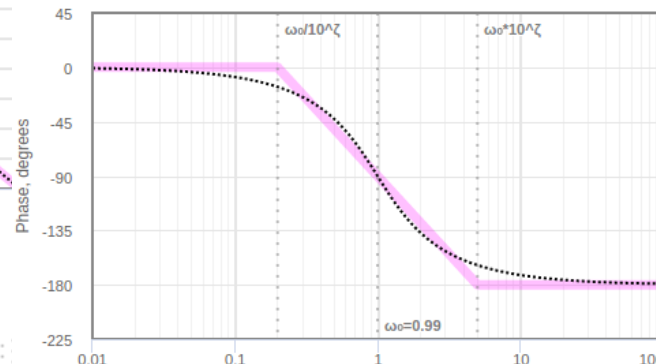

$\zeta = 0.7$

Bode Plot – example

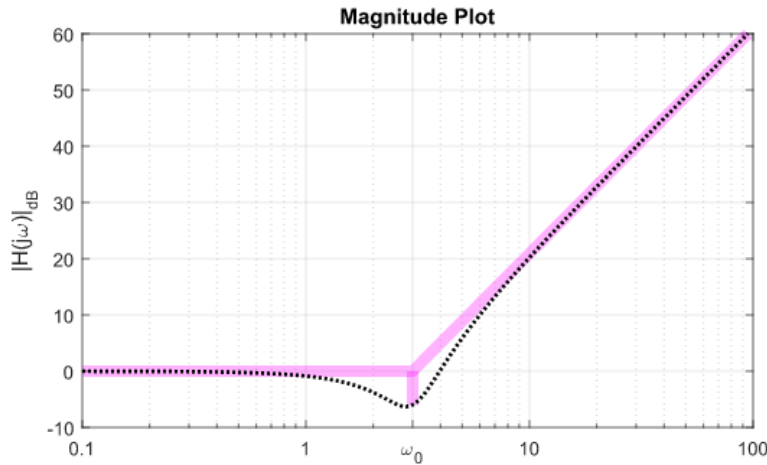


Complex Conjugate Zeros :

Amplitude

- Draw low frequency asymptote at 0 dB
- Draw high frequency asymptote at +40 dB/decade
- If $\zeta < 0.5$, then draw peak at ω_0 with amplitude $|H(j\omega_0)| = +20 \cdot \log_{10}(2\zeta)$, else don't draw peak
- Connect lines

Phase

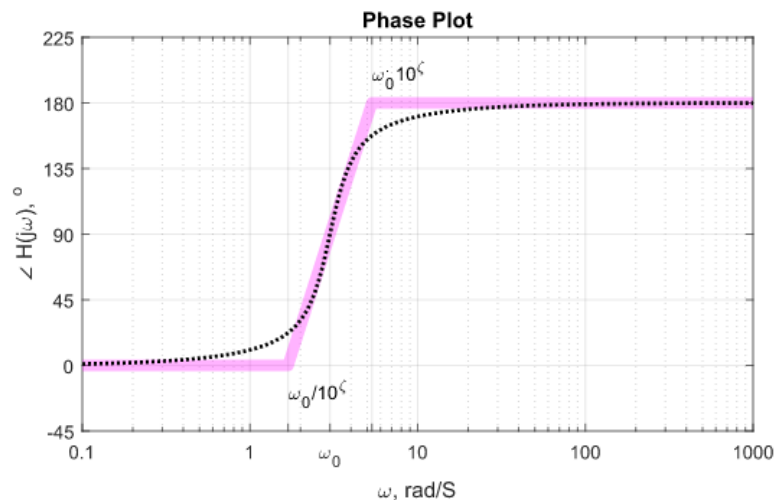- Draw low frequency asymptote at 0°
- Draw high frequency asymptote at $+180^\circ$
- Connect with straight line from $\omega_0 / 10^\zeta$ to $\omega_0 * 10^\zeta$




Bode Plot – example



Asymptotic Bode Plot


$$H(s) = 10 \frac{s + 10}{s^2 + 3s}$$

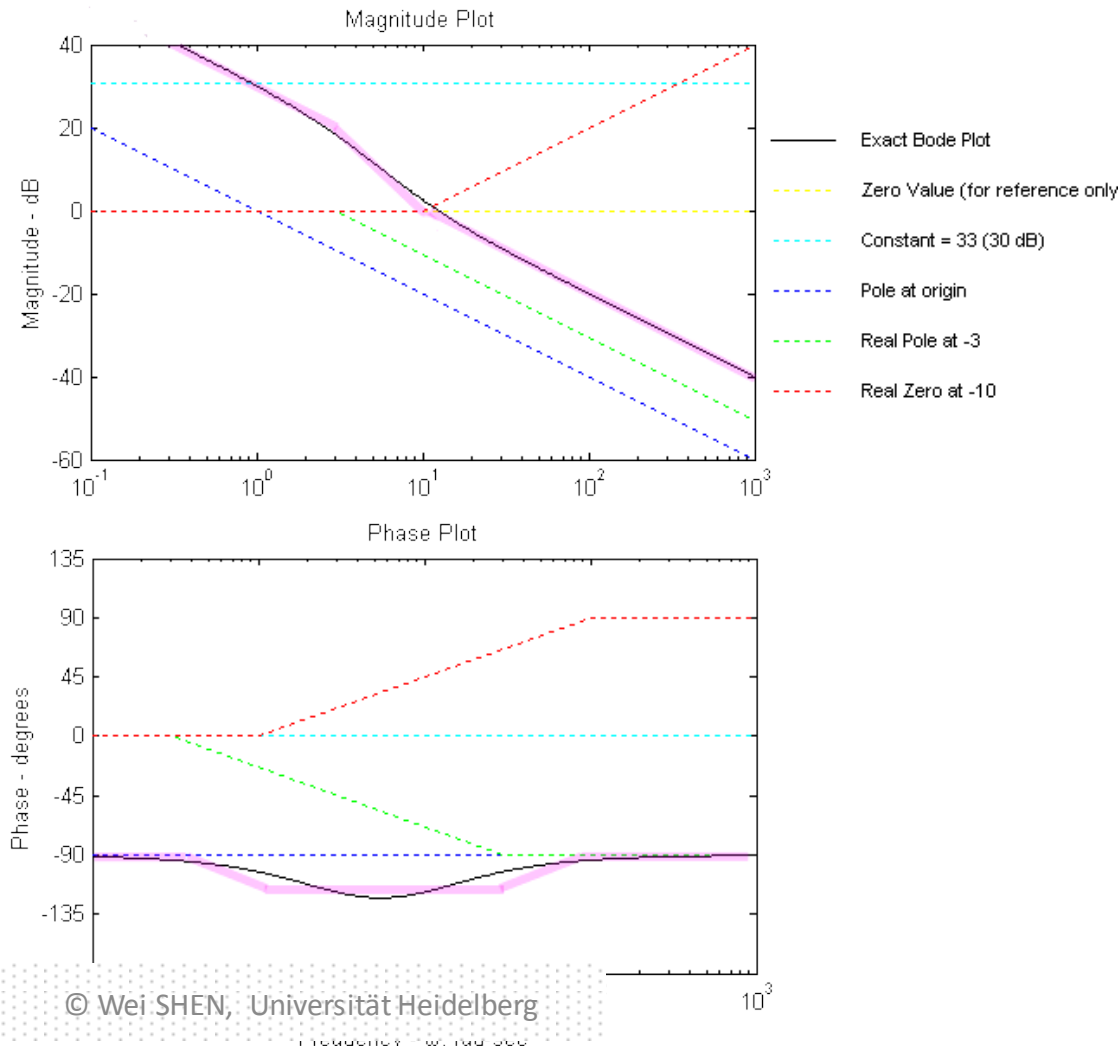

Bode Plot – example



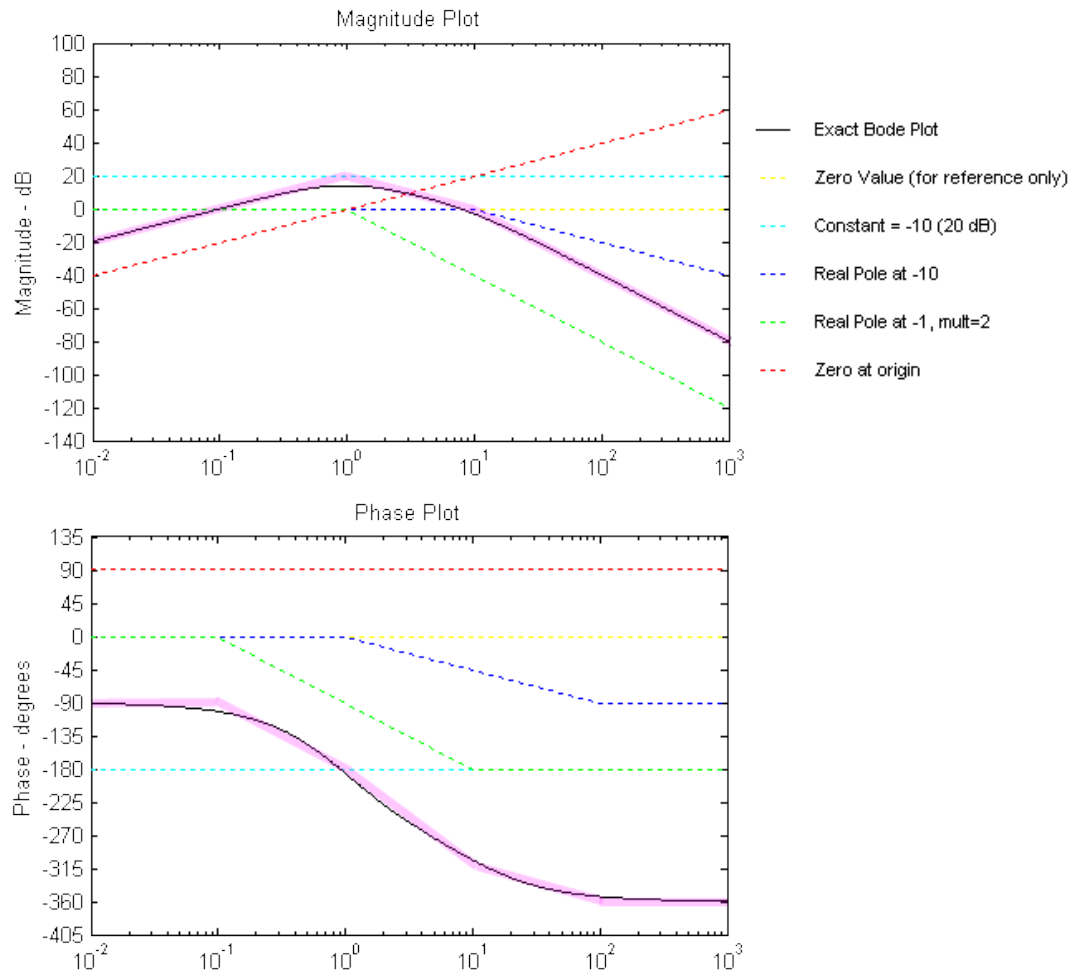Asymptotic Bode Plot $H(s) = -100 \frac{s}{s^3 + 12s^2 + 21s + 10}$






Stability of 2 Pole System



$$H(s) = \frac{A_0 \omega_0^2}{s^2 + 2\zeta \omega_0 s + \omega_0^2} = \frac{A_0}{\left(\frac{s}{\omega_0}\right)^2 + 2\zeta \left(\frac{s}{\omega_0}\right) + 1}$$

Transfer Function : $\frac{A_{out}}{A_{in}}$


Root Locus

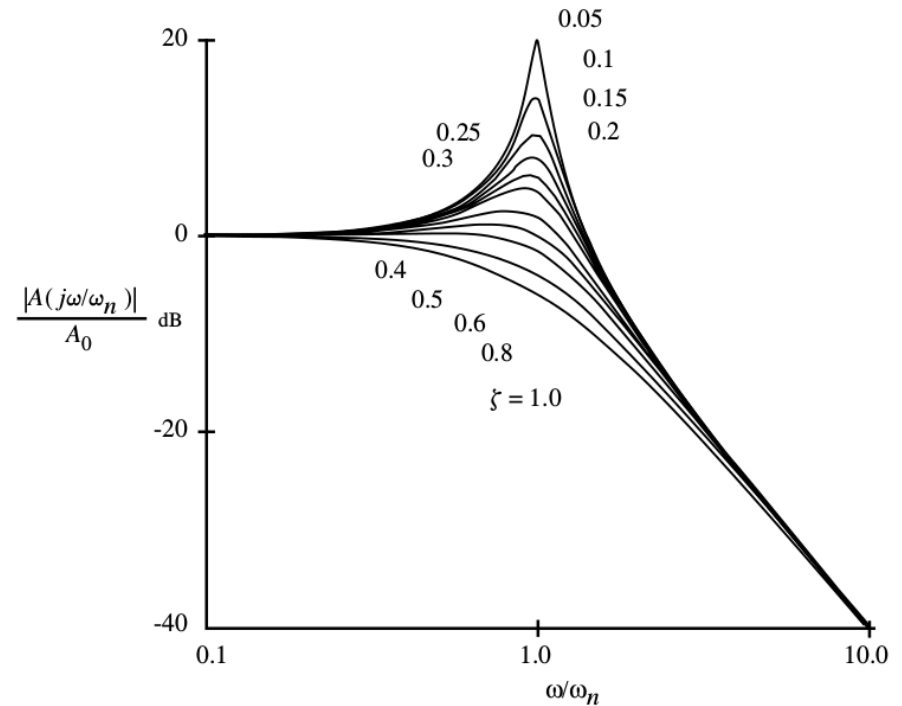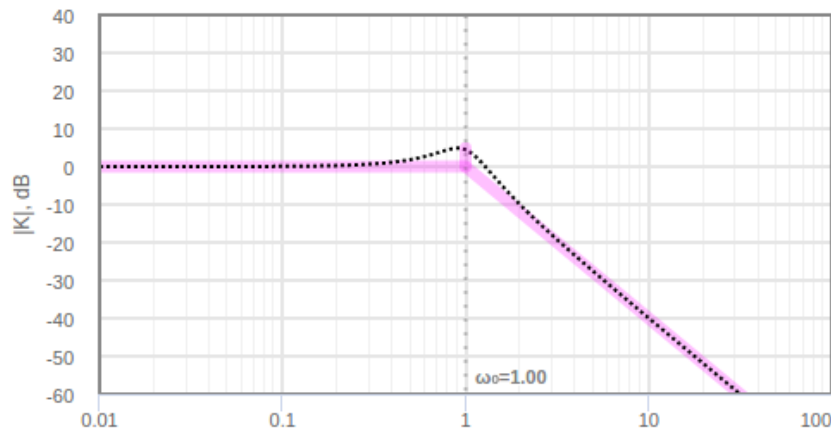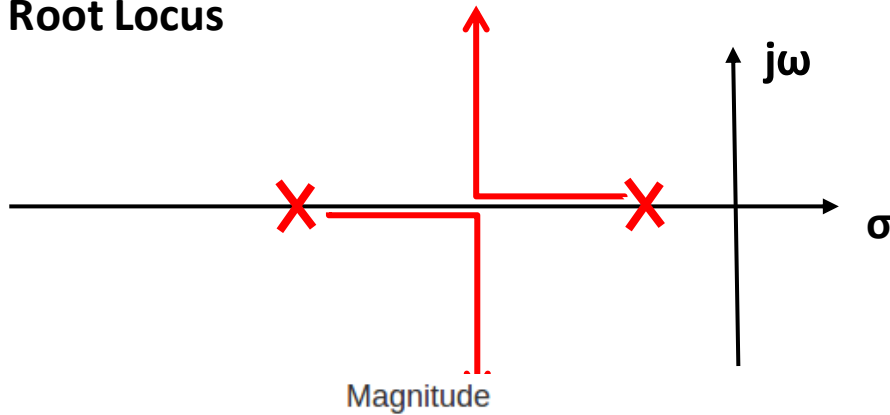

Stability of 2 Pole System



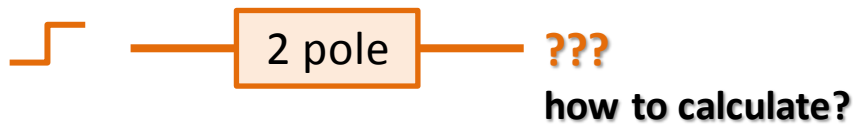
- **Unit Step Response** in the time domain



$$v_o(t) = A_0 \left[1 - \frac{1}{\sqrt{1-\zeta^2}} e^{-\zeta\omega_n t} \sin\left(\sqrt{1-\zeta^2} \omega_n t + \phi\right) \right]$$

with
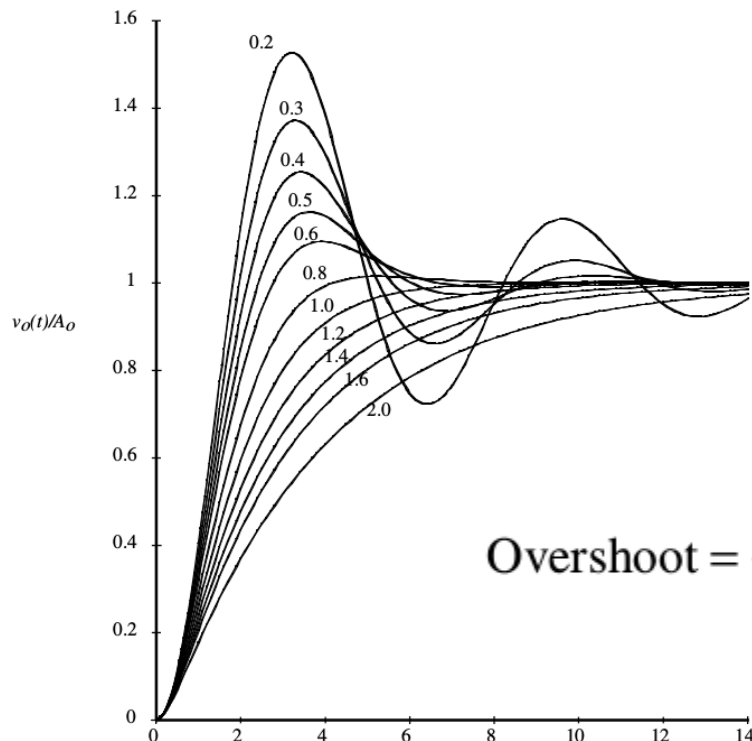
$$\phi = \tan^{-1} \left(\frac{\sqrt{1-\zeta^2}}{\zeta} \right)$$



As $\zeta \rightarrow 0$, the unit step response oscillate
Usually, ζ is set to 0.7 – 0.8 to enhance response speed


$$\text{Overshoot} = \frac{\text{Peak value} - \text{Final value}}{\text{Final value}} = \exp\left(\frac{-\pi\zeta}{\sqrt{1-\zeta^2}}\right)$$

What about a impulse response ??????


Stability of 2 Pole System



What about a impulse response ??????

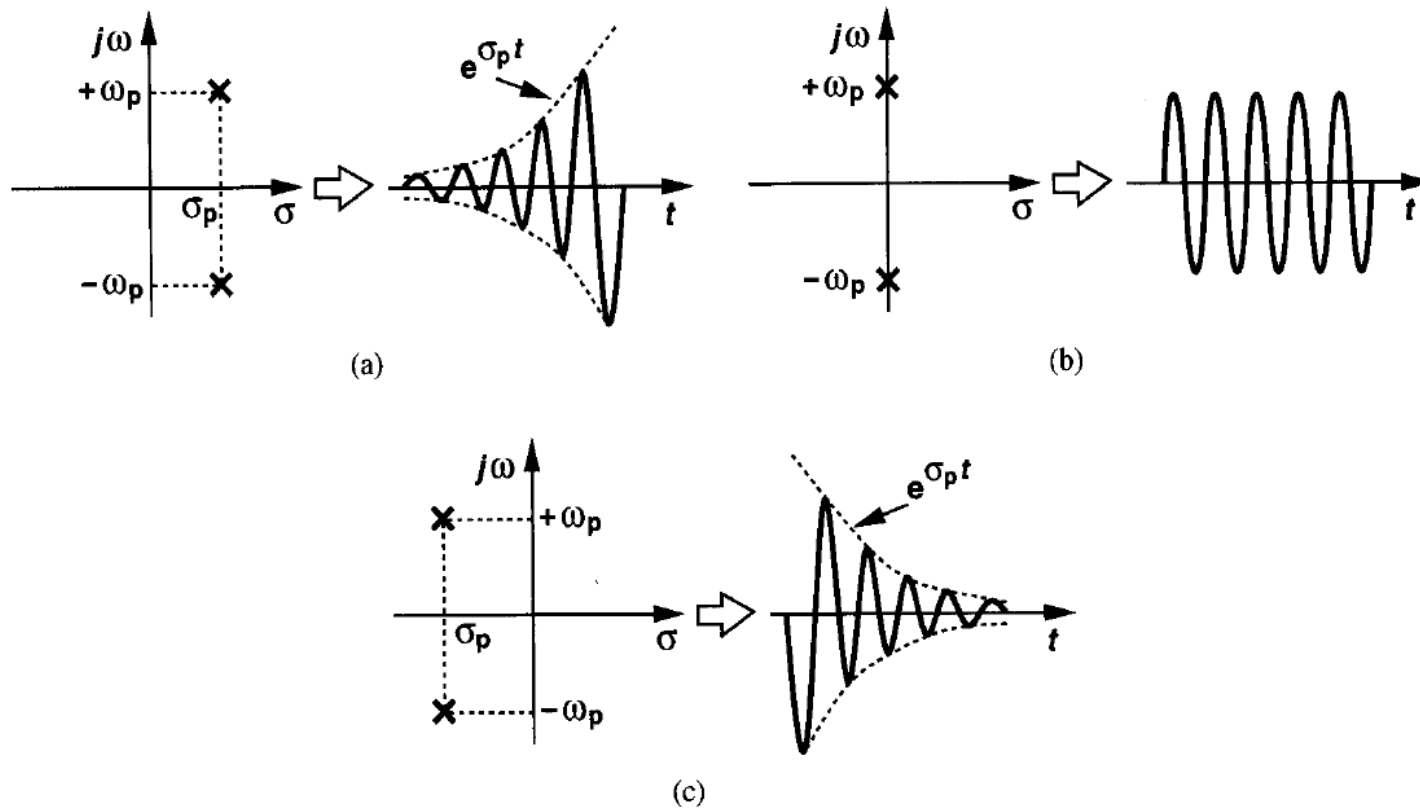

Stability of Feedback Systems

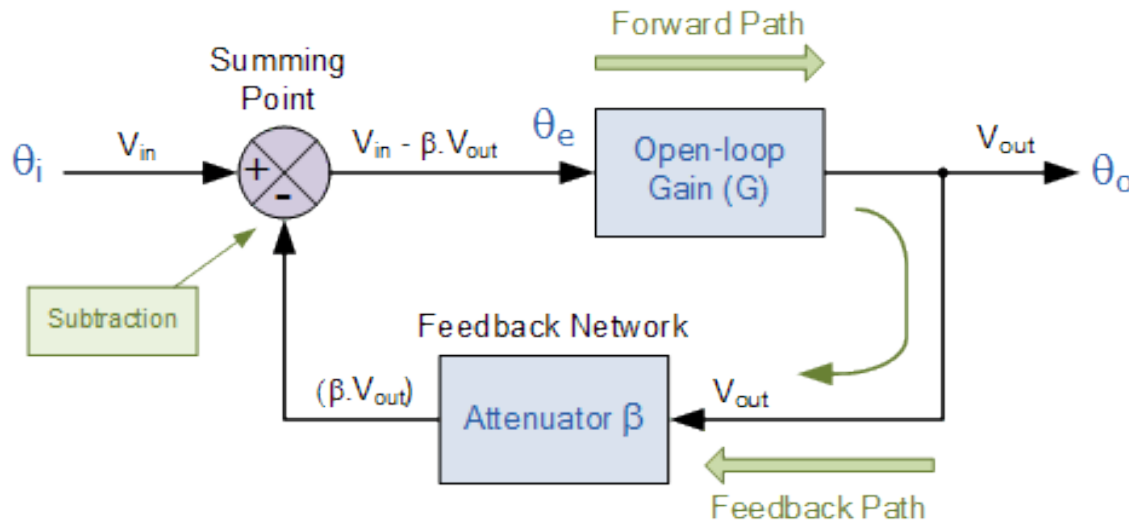

$$\frac{Y}{X}(s) = \frac{H(s)}{1 + \beta H(s)},$$

$$\beta \leq 1$$

If $\beta H(s) = -1$, then the transfer function goes to infinity which means:

@ certain frequency, $|\beta H(j\omega_0)| = 1$ & $\angle \beta H(j\omega_0) = -180^\circ$

In total, 360° phase shift, as negative feedback is used
Oscillation builds up with 360° feedback and **positive amplitude**
the amplitude feedbacked should be more than unity



Stability of Feedback Systems



$$\frac{Y}{X}(s) = \frac{H(s)}{1 + \beta H(s)},$$

the frequency response of $\beta H(s)$ is always used to indicate the stability of the system

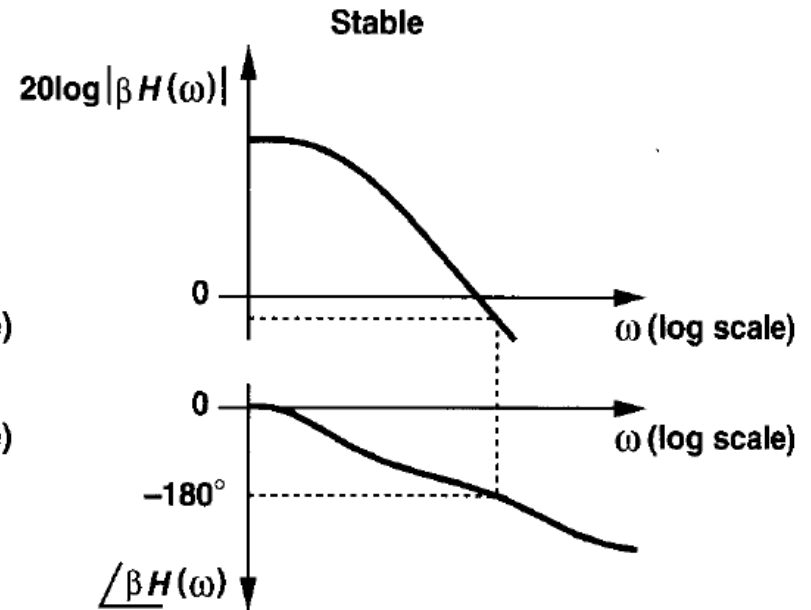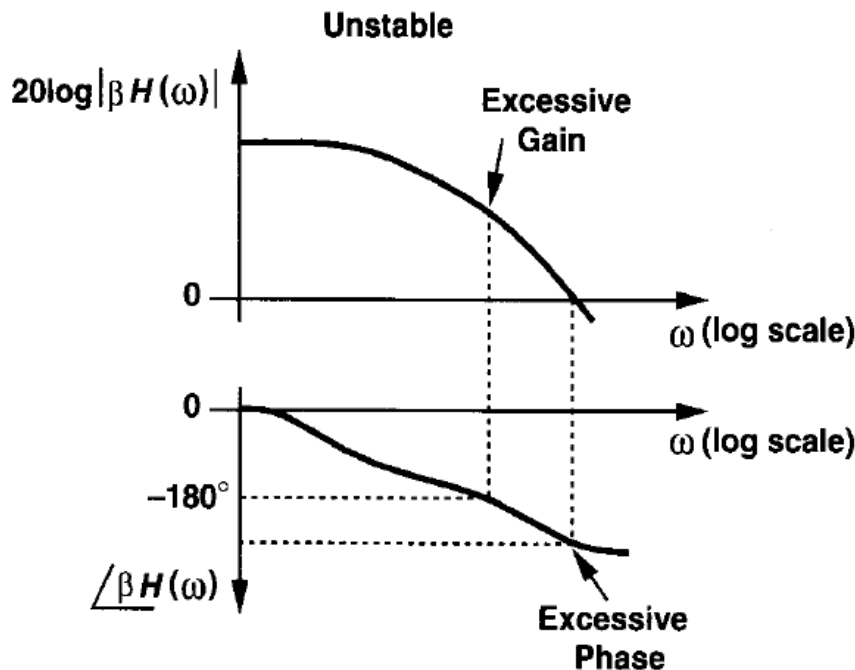
by knowing the $\beta H(s)$, already able to tell the stability



Stability of Feedback Systems







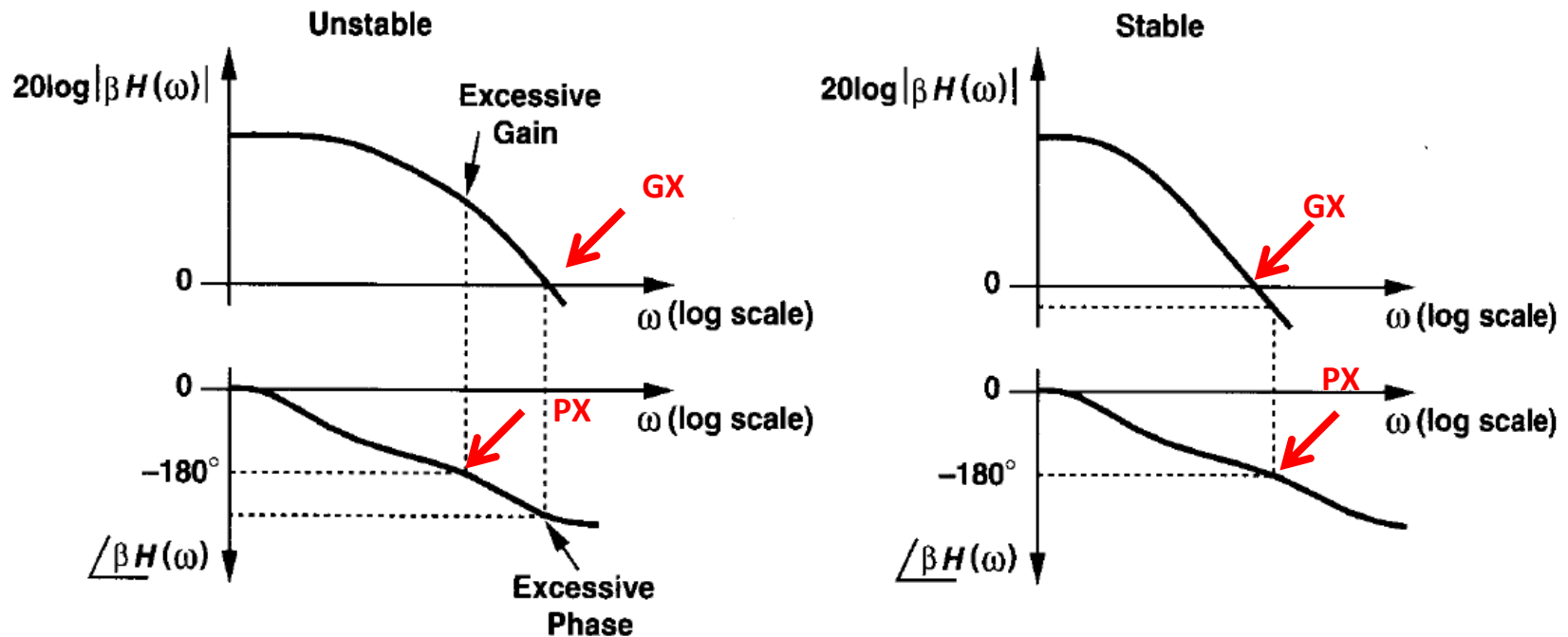- Definition : Gain-crossover (GX), Phase-crossover (PX)



Stability \rightarrow GX earlier than PX (phase margin) , or
@ GX, phase shift less than -180° , or @PX Gain less than unity

Stability of Feedback Systems

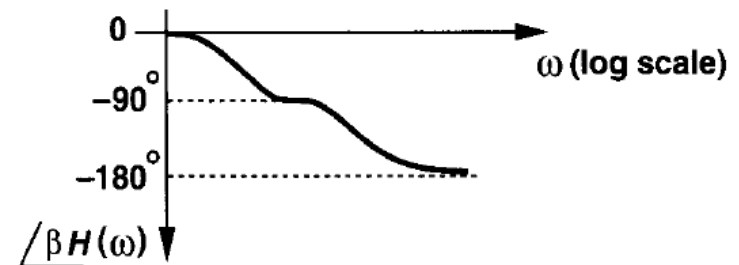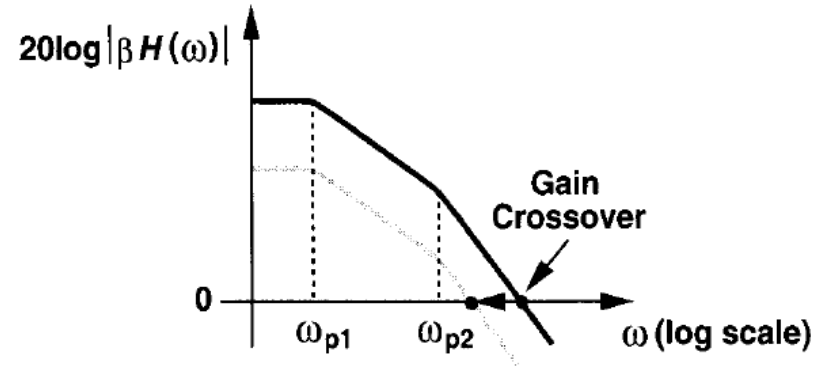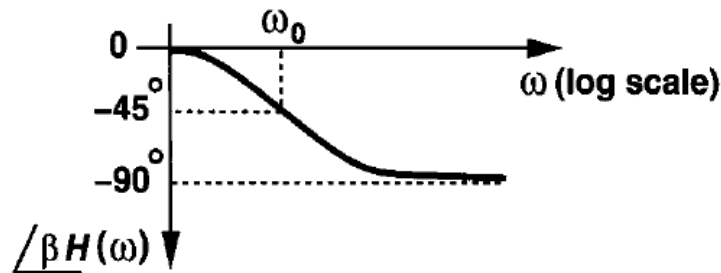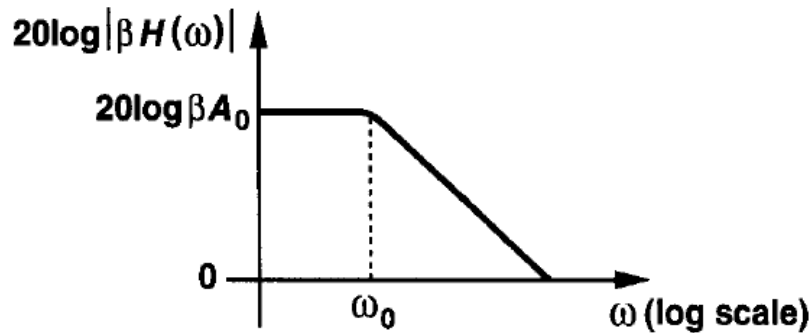

Single Pole will not create phase shift greater than 90, hence always stable



2 Pole system will also be stable but with phase margin concern, Multiple Pole system will start to be instable

$\beta = 1$ is the worst condition, because, for $\beta < 1$, the GX moves leftwards, GX stays


Stability of Feedback Systems



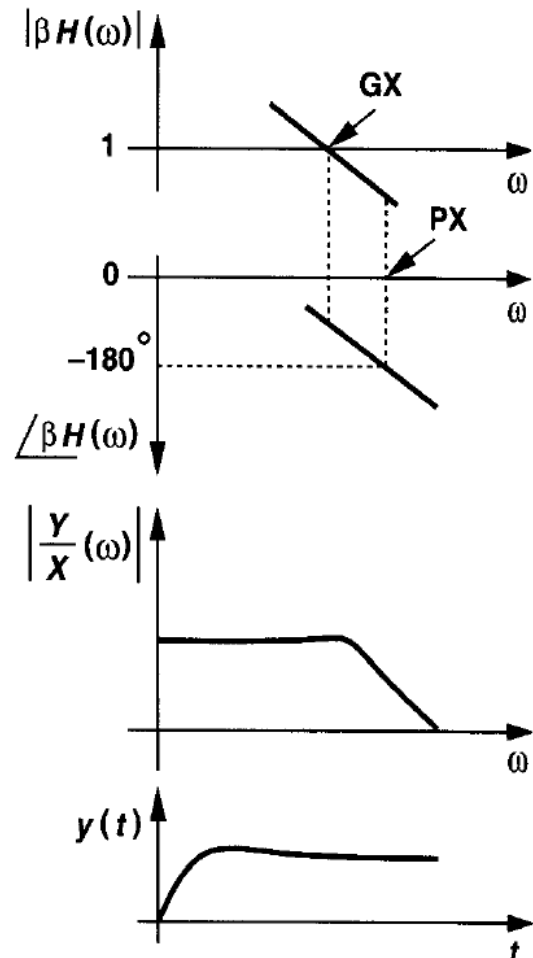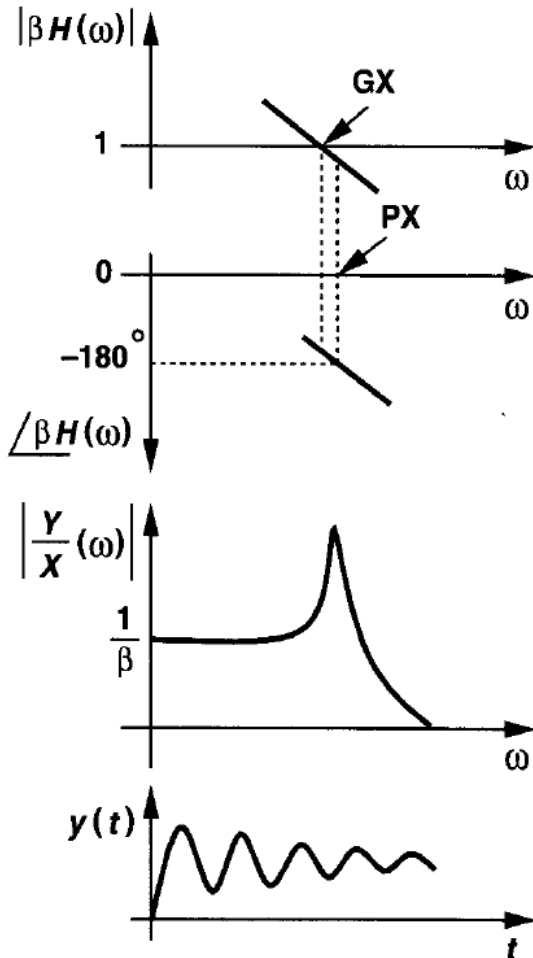phase margin: how far away are GX ahead of PX



unit step response
of 2 pole systems

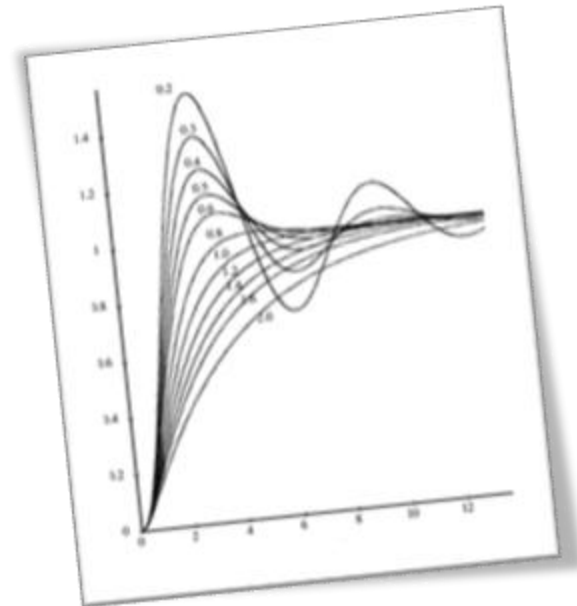


Stability of Feedback Systems




phase margin : how far away are GX ahead of PX
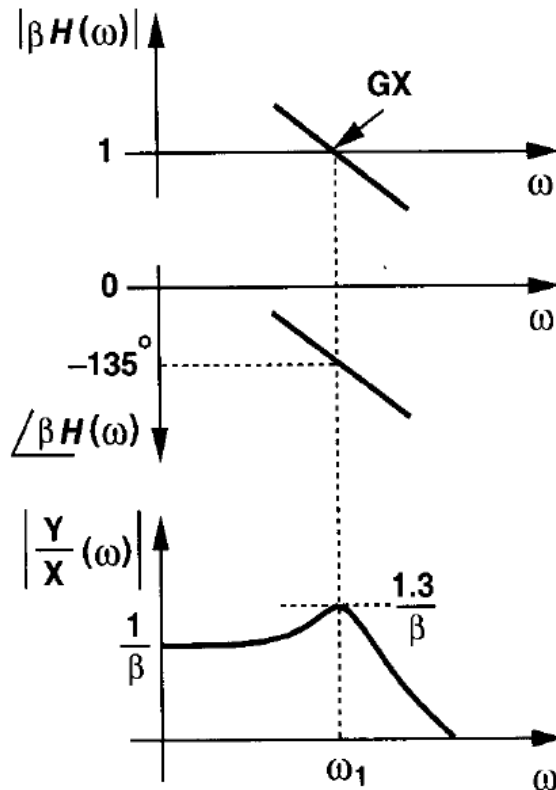
$$\frac{Y}{X}(j\omega) = \frac{H(j\omega)}{1 + \beta H(j\omega)}$$






@ GX , $\beta H(j\omega) = 1 \cdot \exp [-j (180^\circ - \text{PMargin})]$

Stability of Feedback Systems

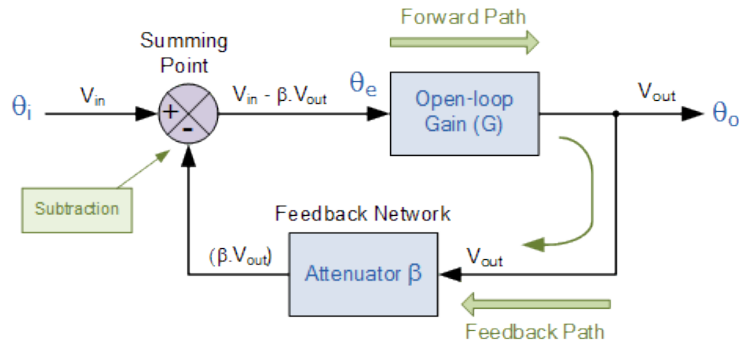

unit step response of feedback system,
with different phase margin

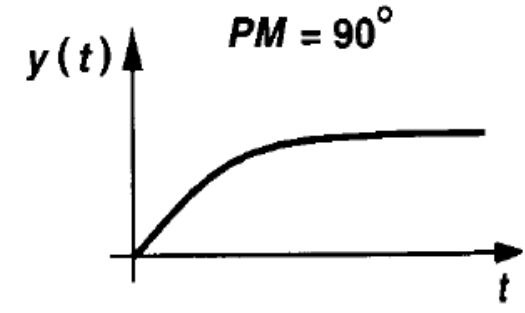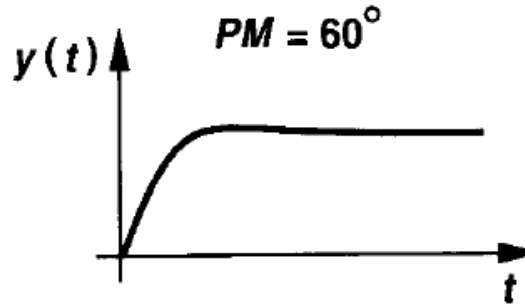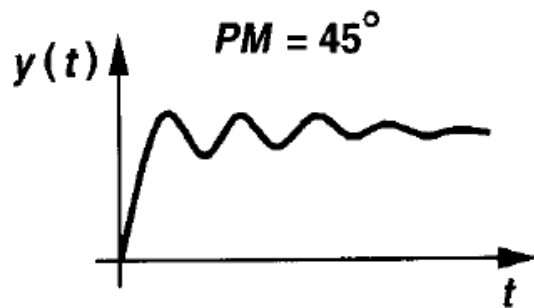usually set @ 60° for no over&undershoot
same as the 2 pole system transfer function
c.f. page 12





even though the 2 pole system is stable, it has the phase margin problem, the relative location of the first and second poles determines the phase margin ... c.f. the example on next page

Stability of Feedback Systems



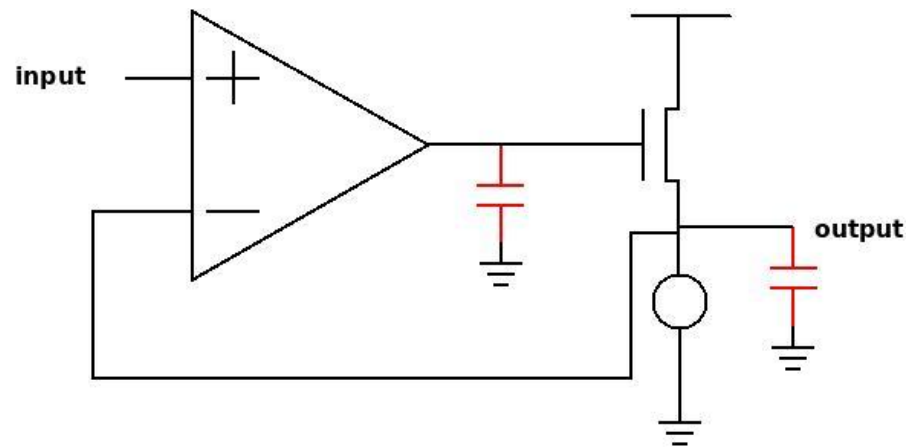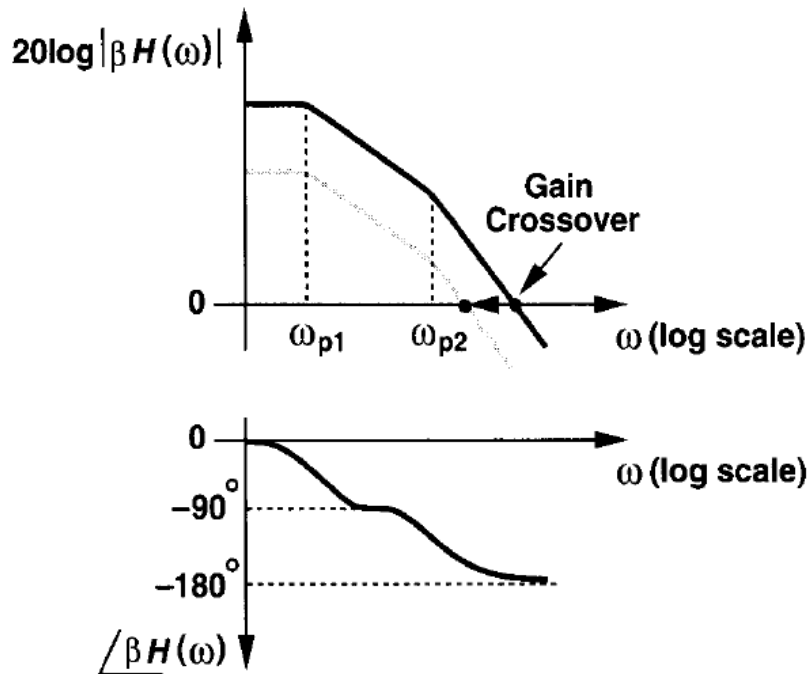even though the 2 pole system is stable, it has the phase margin problem, the relative location of the first and second poles determines the phase margin



source follower is used to drive a large capacitive load, then the phase margin needs to be considered



however, all the analysis is based on small-signal
large signal will also ring even if small signal has
enough phase margin!!!

Compensation of 1 stage Amp



2 ways of compensating 1 stage Amp :

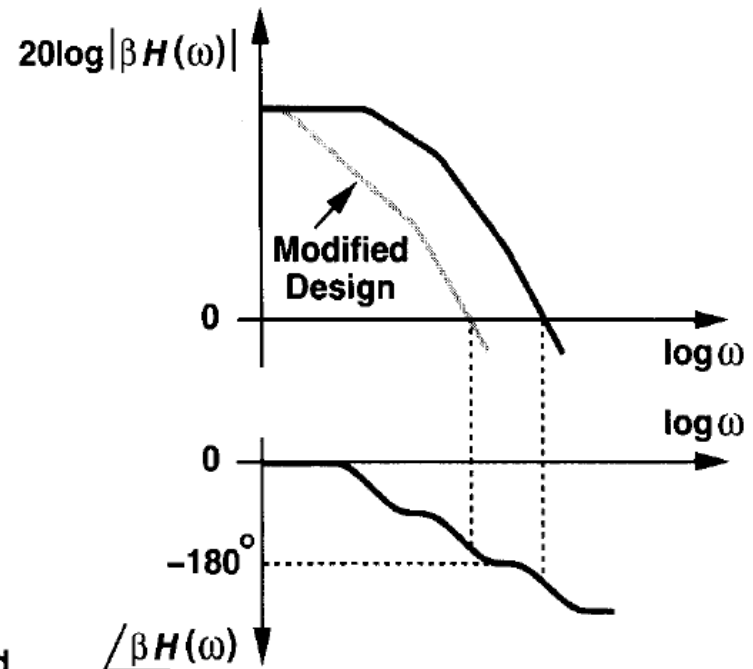
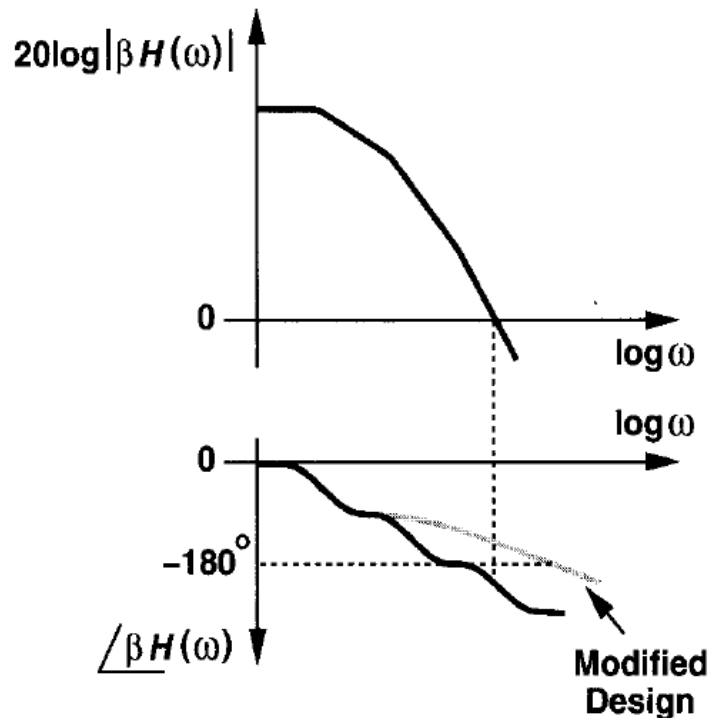
- ✓ reducing the amount of poles (less phase shift)
- ✓ moving dominant pole towards origin



Compensation of 1 stage Amp




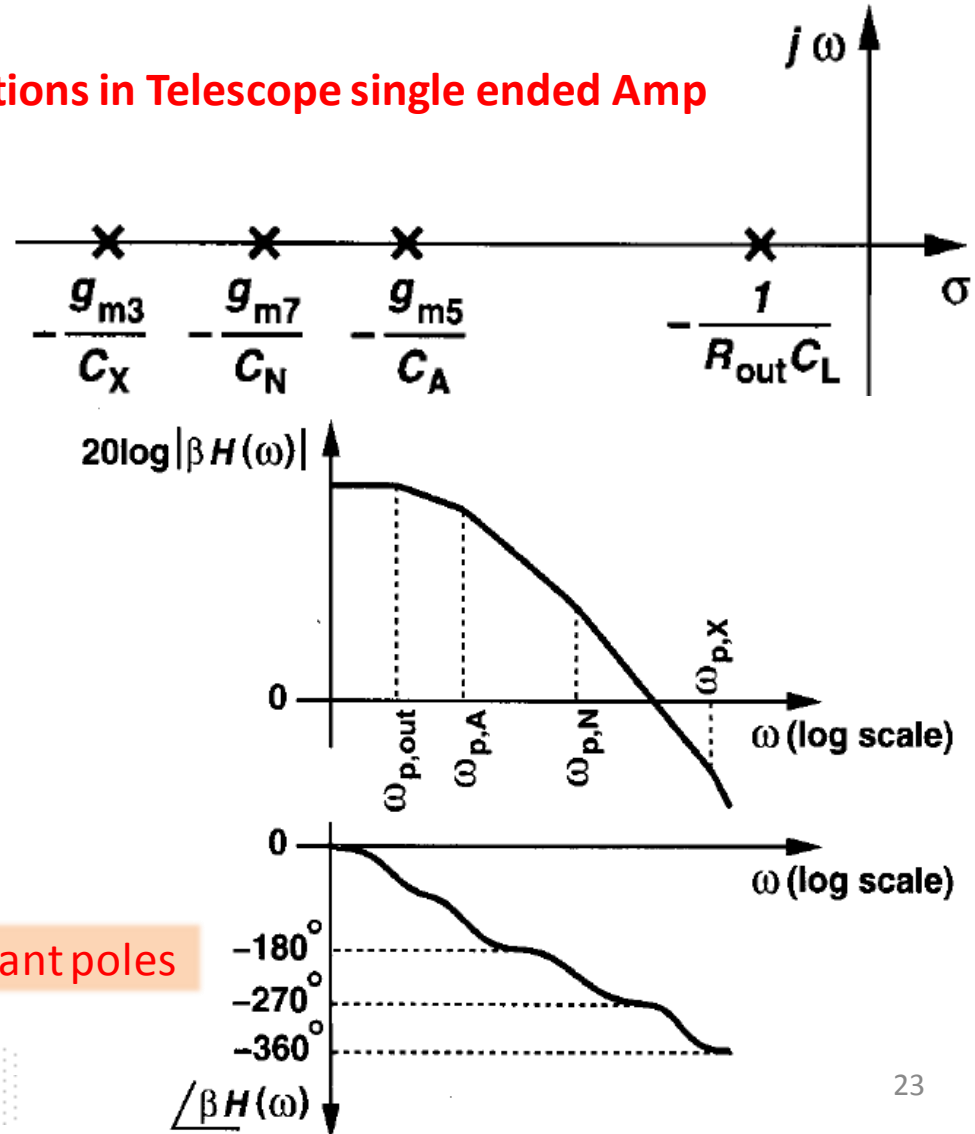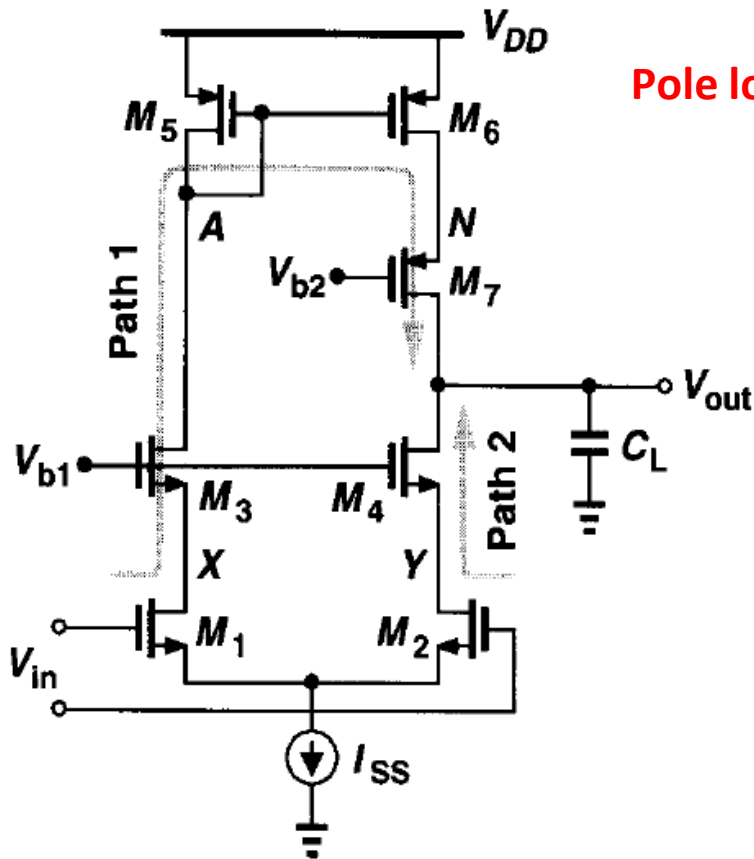Pole locations in Telescope single ended Amp




stability is a concern as for the non-dominant poles



Compensation of 1 stage Amp

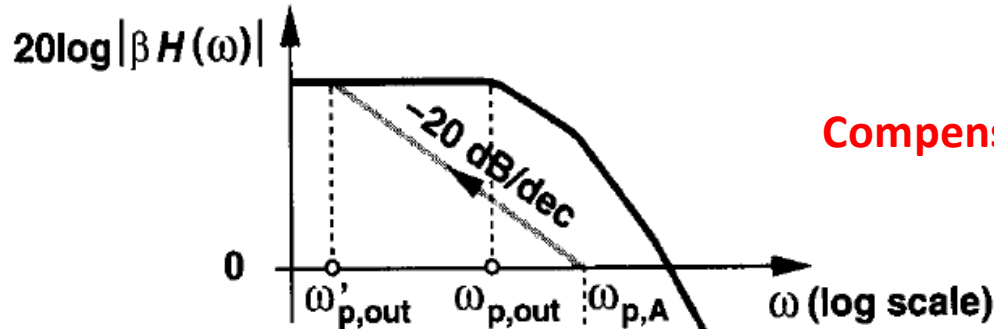

Compensating with larger C_{load}



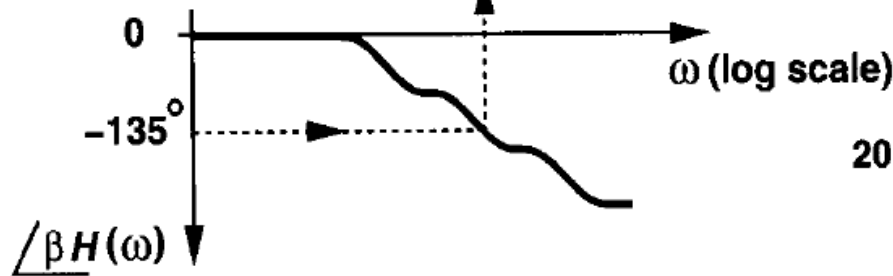


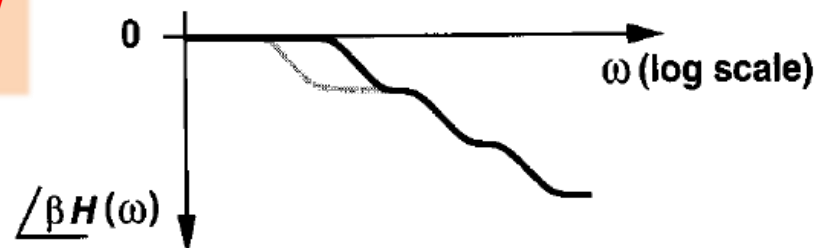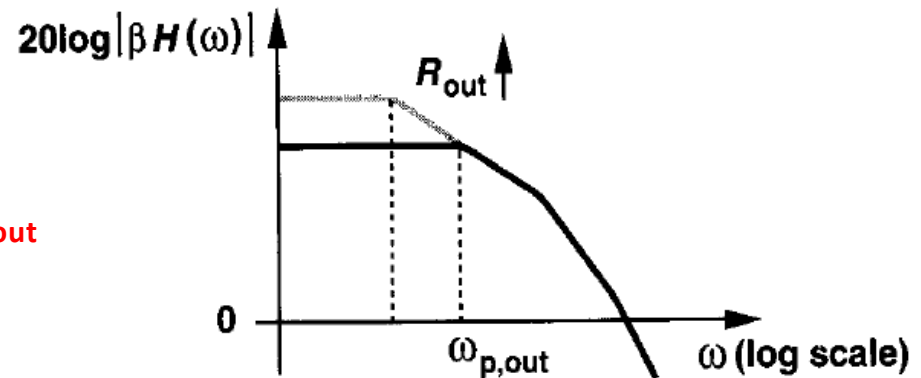Compensation not valid with larger R_{out}



non-dominant poles need to be pushed above GBW depending on the phase margin required

Compensation of 1 stage Amp

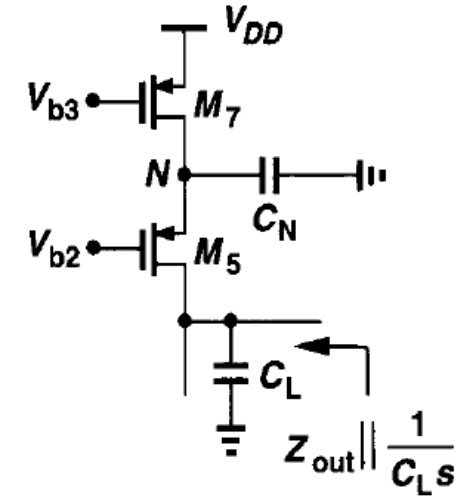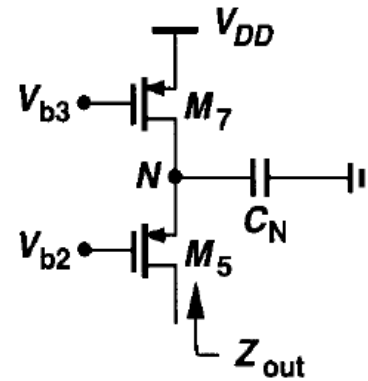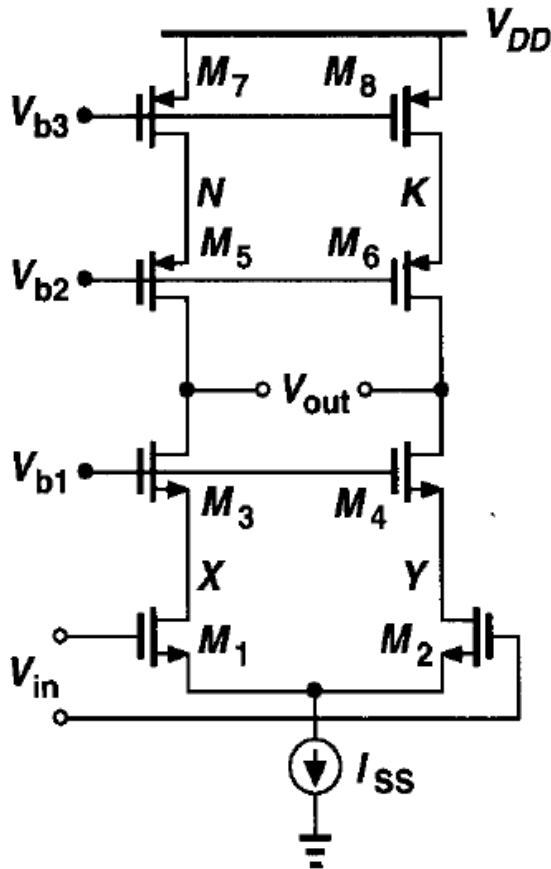


$$Z_{out} \parallel \frac{1}{C_{LS}} = \frac{(1 + g_{m5}r_{O5}) \frac{r_{O7}}{r_{O7}C_{NS} + 1} \cdot \frac{1}{C_{LS}}}{(1 + g_{m5}r_{O5}) \frac{r_{O7}}{r_{O7}C_{NS} + 1} + \frac{1}{C_{LS}}}$$



$$= \frac{(1 + g_{m5}r_{O5})r_{O7}}{[(1 + g_{m5}r_{O5})r_{O7}C_L + r_{O7}C_N]s + 1}$$

similar for fully-differential telescope structure
but the poles at N and K are invisible or merged
into the output pole



Compensation of 2 stage Amp

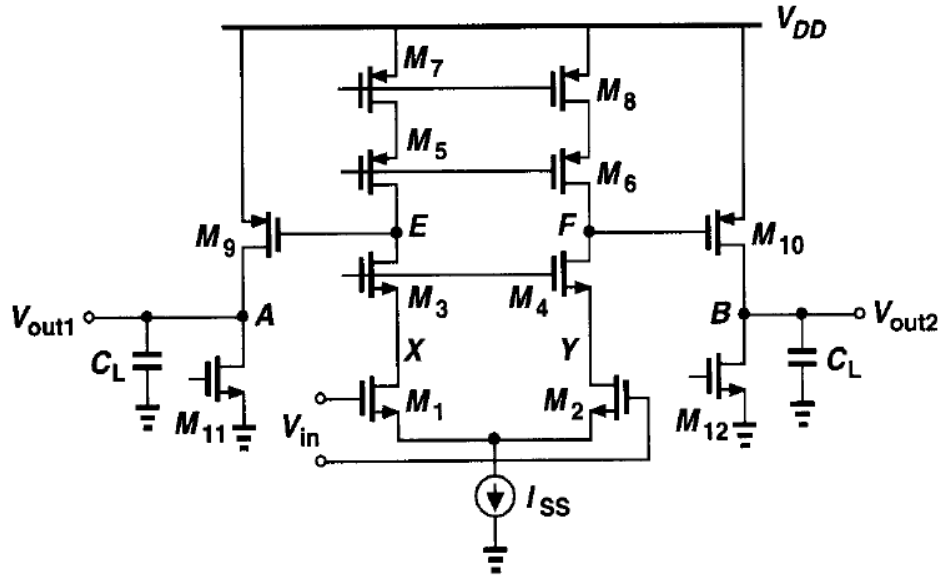


Pole locations in 2 stage Amps

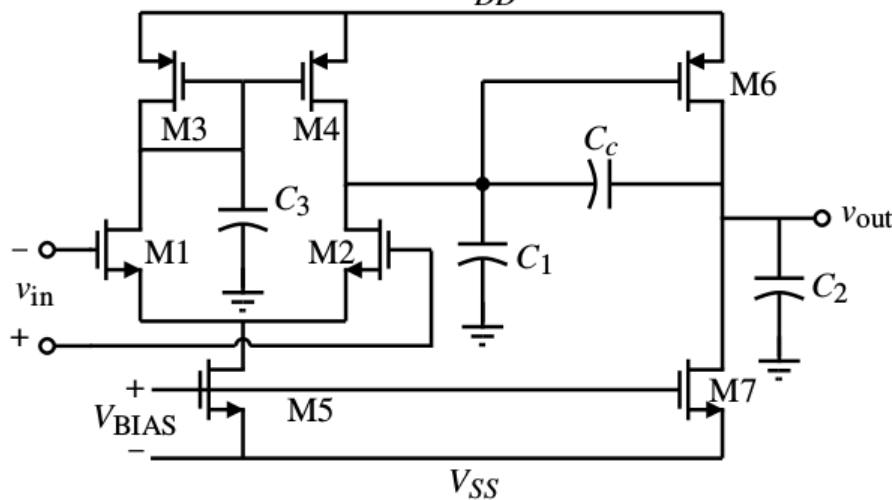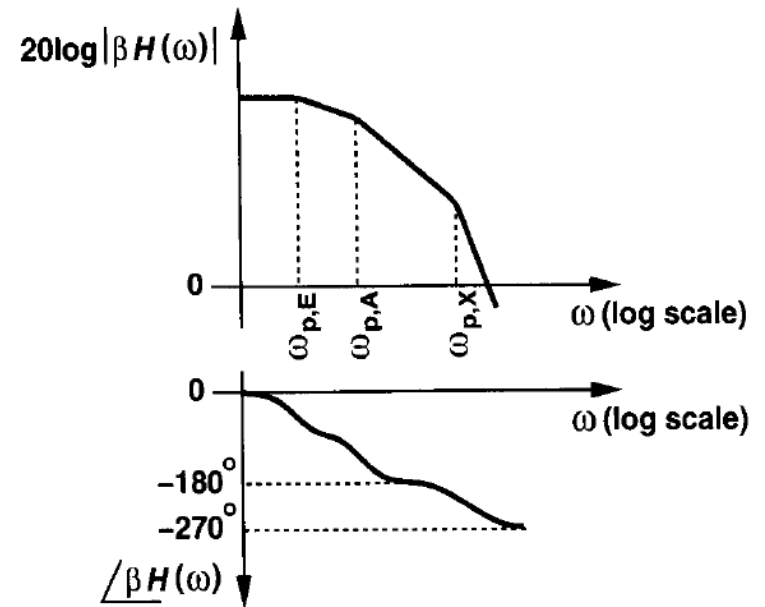


Compensation of 2 stage Amp

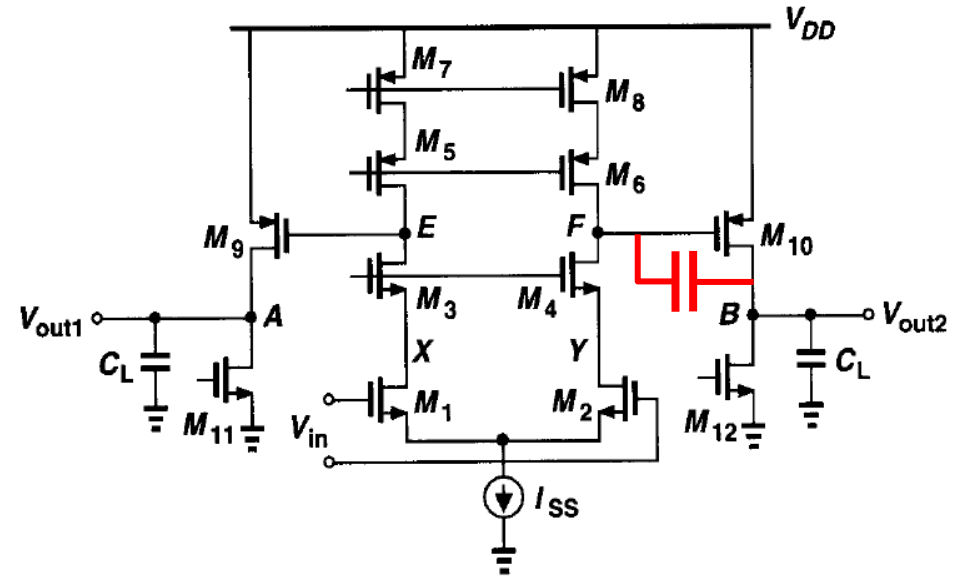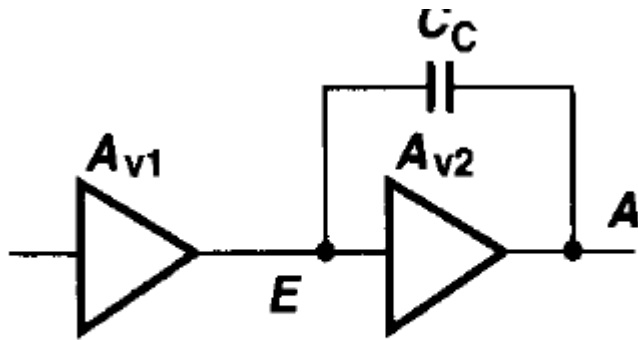

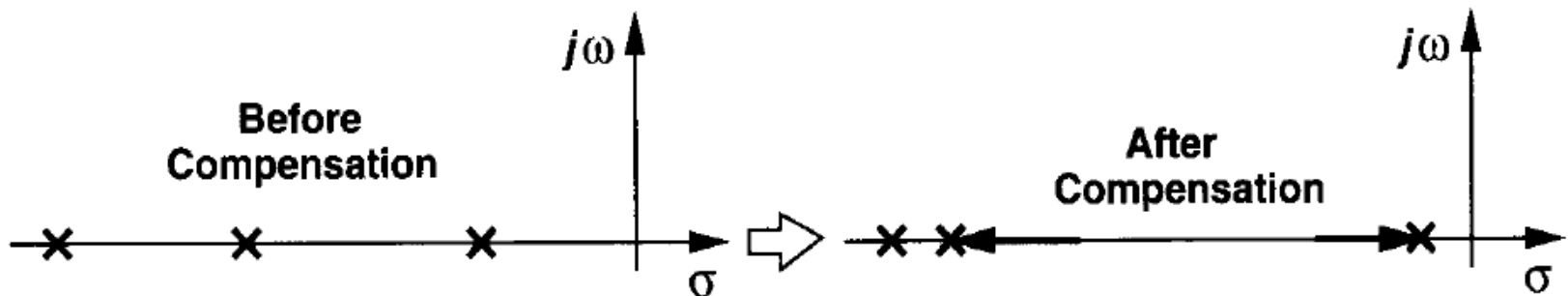the effect of Miller Capacitor :
remember the Miller Effects from single CS stage




Compensation of 2 stage Amp

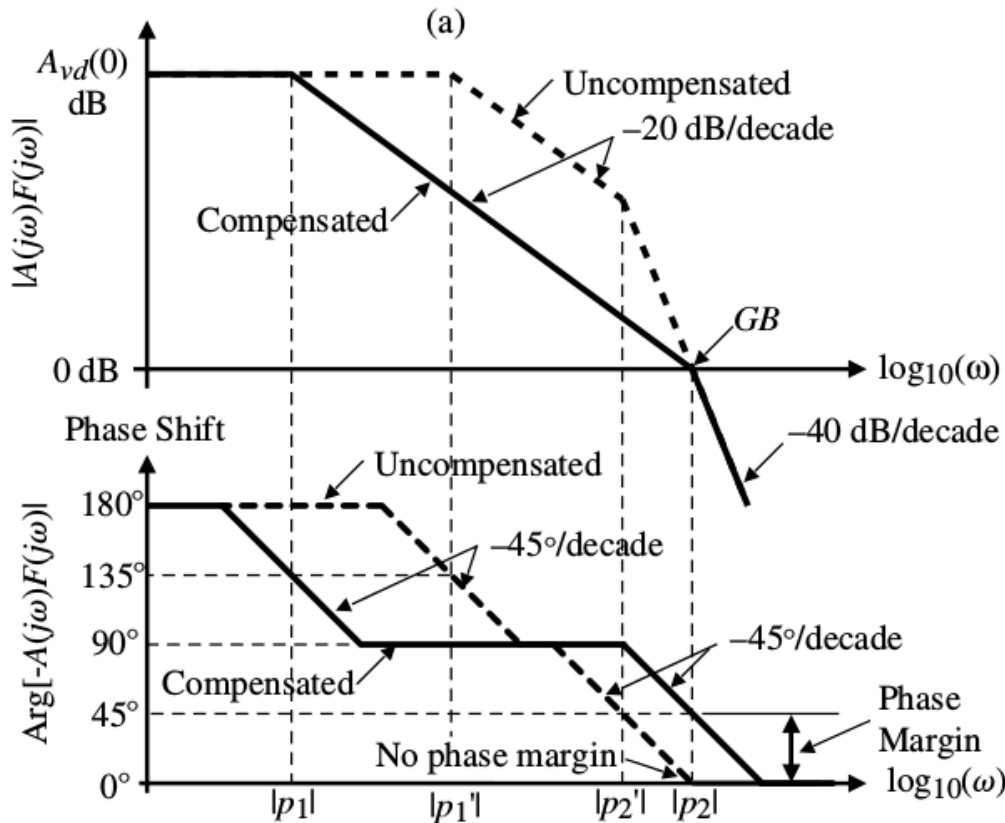

what we want to achieve with
Miller Compensation

Ideal Case but with side effects

Compensation of 2 stage Amp

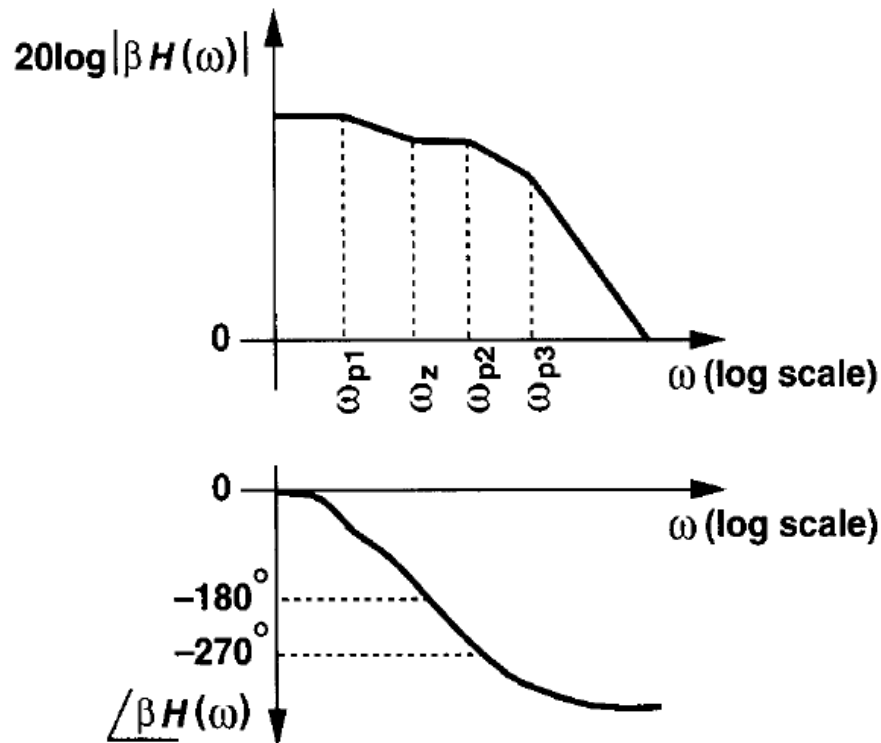



Effects of the RHP Zero, kills the phase margin, even though extends the bandwidth

Or it has to be placed carefully away from GBW

e.g. If RHP Zero placed at 10 times GBW, in order to achieve 60° phase margin


the second pole must be placed at least 2.2 times higher than GBW

Compensation of 2 stage Amp

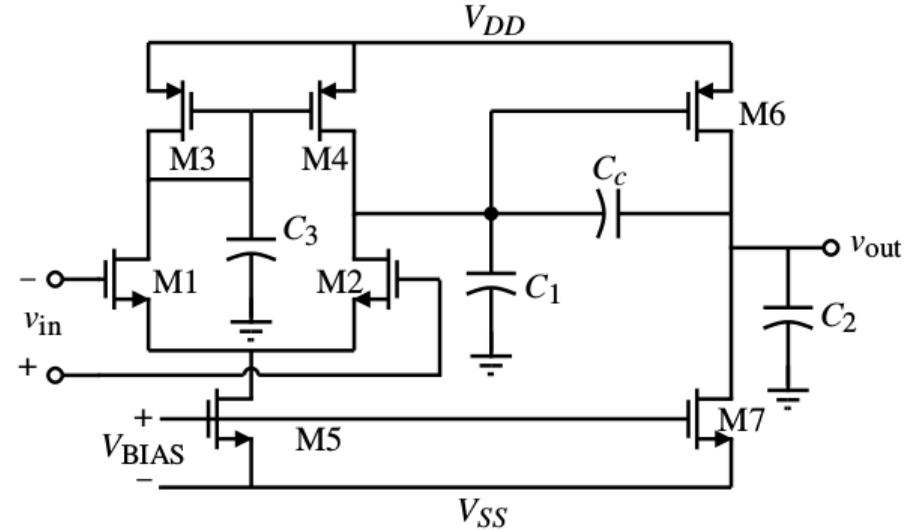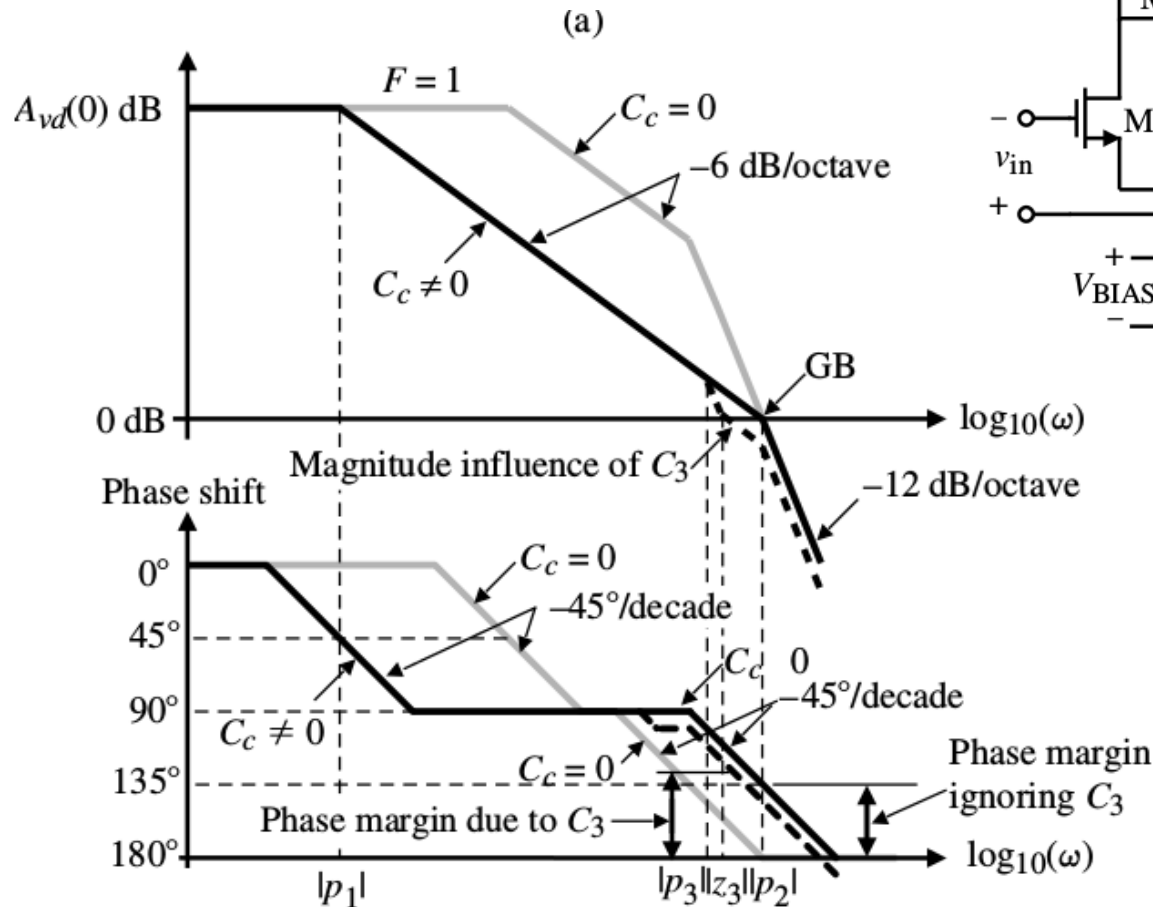

the effects of the Mirror Poles and zeros , marked at p_3 and z_3

Compensation of 2 stage Amp

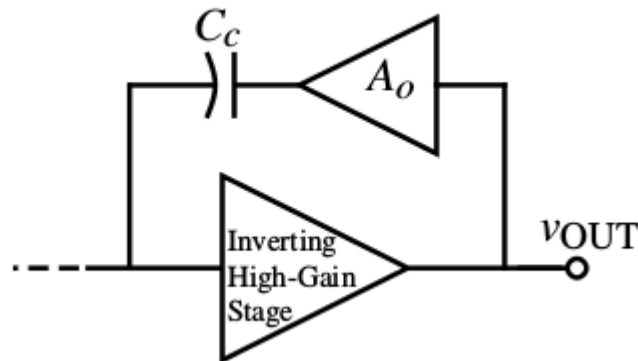

how to remove the RHP zero,
feedback amplifier with $R_o = 0$

$$\frac{V_o(s)}{V_{in}(s)} = \frac{(g_{mI})(g_{mII})(R_I)(R_{II})}{1 + s[R_I C_I + R_{II} C_{II} + R_I C_c + g_{mII} R_I R_{II} C_c] + s^2[R_I R_{II} C_{II} (C_I + C_c)]}$$

$$p_1 \cong \frac{-1}{R_I C_I + R_{II} C_{II} + R_I C_c + g_{mII} R_I R_{II} C_c} \cong \frac{-1}{g_{mII} R_I R_{II} C_c}$$

$$p_2 \cong \frac{-g_{mII} C_c}{C_{II} (C_I + C_c)}$$

$$p_4 \cong \frac{-1}{R_o [C_I C_c / (C_I + C_c)]}$$

if R_o present


$$z_2 \cong \frac{-1}{R_o C_c}$$

Compensation of 2 stage Amp



using nulling Resistance
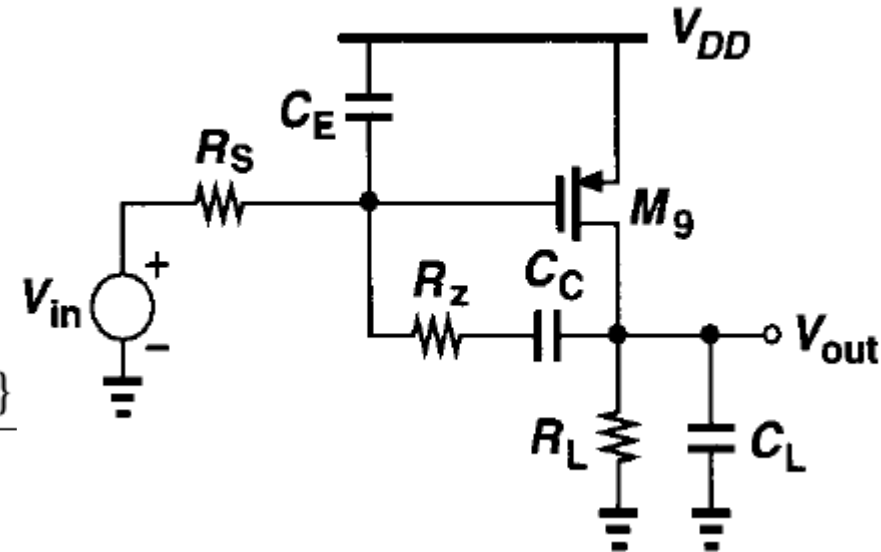
$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{a\{1 - s[(C_c/g_{mII}) - R_z C_c]\}}{1 + bs + cs^2 + ds^3}$$



a ^{with} $g_{mI}g_{mII}R_I R_{II}$

$$b = (C_{II} + C_c)R_{II} + (C_I + C_c)R_I + g_{mII}R_I R_{II} C_c + R_z C_c$$

$$c = [R_I R_{II}(C_I C_{II} + C_c C_I + C_c C_{II}) + R_z C_c (R_I C_I + R_{II} C_{II})]$$

$$d = R_I R_{II} R_z C_I C_{II} C_c$$

Compensation of 2 stage Amp



$$p_1 \cong \frac{-1}{(1 + g_{mII}R_{II})R_I C_c} \cong \frac{-1}{g_{mII}R_{II}R_I C_c}$$

$$p_2 \cong \frac{-g_{mII}C_c}{C_I C_{II} + C_c C_I + C_c C_{II}} \cong \frac{-g_{mII}}{C_{II}}$$


$$p_4 = \frac{-1}{R_z C_I}$$

$$z_1 = \frac{1}{C_c(1/g_{mII} - R_z)}$$

using nulling Resistance to
cancel out the p_2 , such that
only the p_3 and p_4 remains

the bandwidth can be extended

Compensation of 2 stage Amp


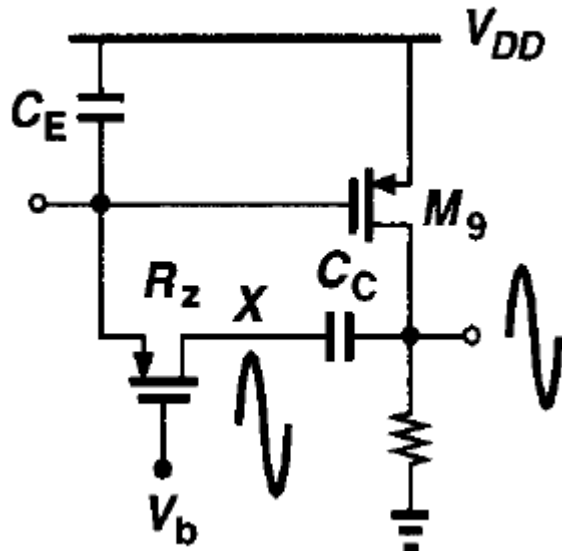


however problems:



$$R_z = \frac{C_L + C_c}{g_{m9} C_c}$$

Depending on C_L , needs to be flexible

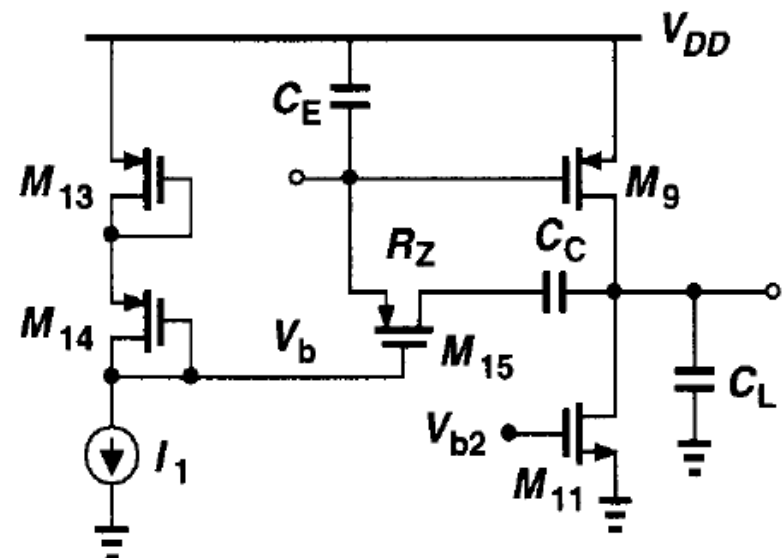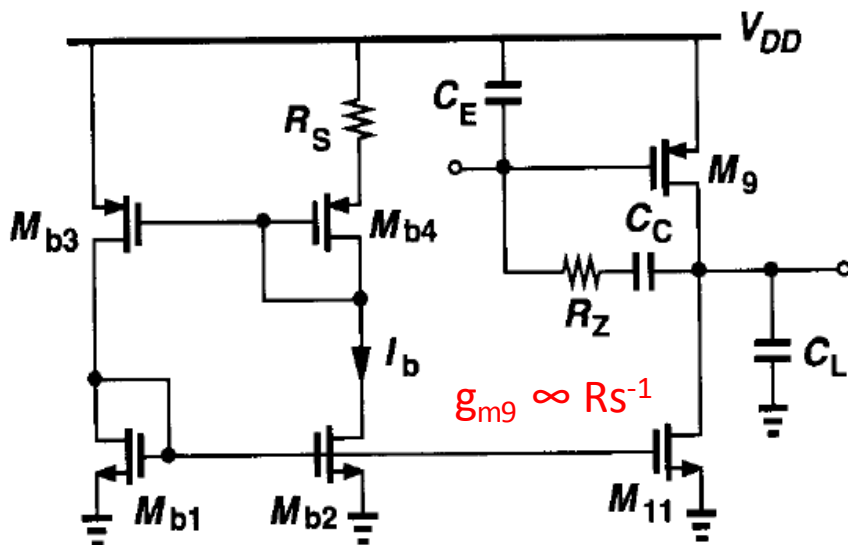use the triode transistor to replace R_z ,
but swing effect for fixed C_L ,
 V_b anti-affect the process variation



Compensation of 2 stage Amp

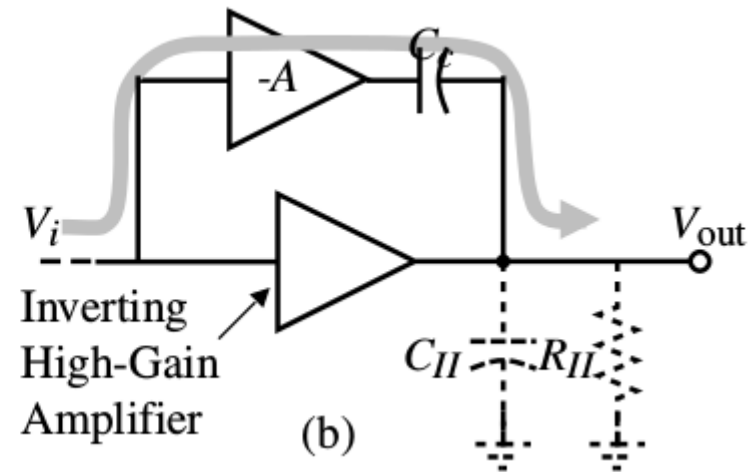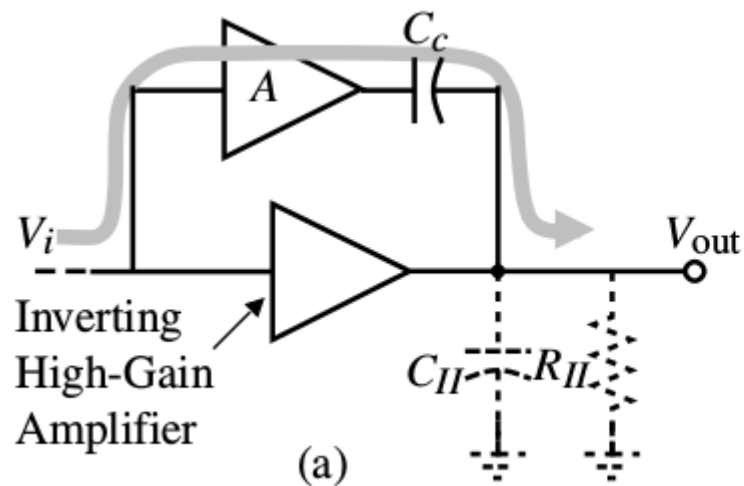


feedforward : moving the RHP zero to LHP zero

Compensation of 2 stage Amp



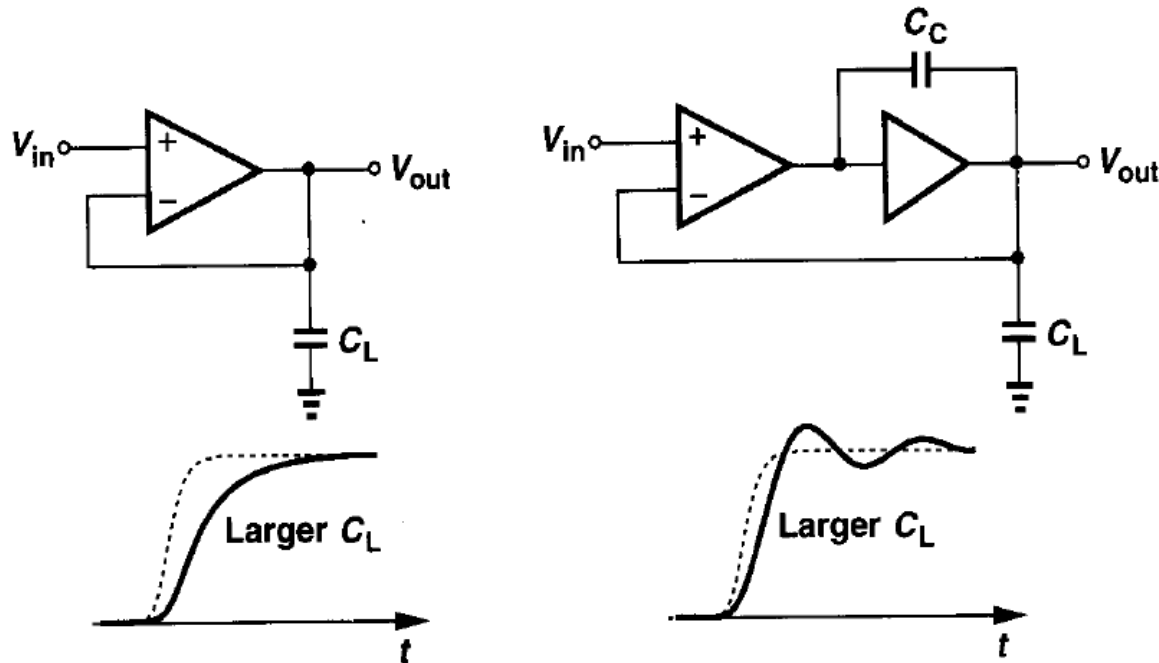phase margin with different C_{load} and pole swapping!!!



***what if the Loading Capacitor is extremely large,
then the poles are swapping
how does it look like ?***